

ADVANCED ELECTRICAL CIRCUIT BETI 1333

SECOND ORDER SOURCE-FREE SERIES RLC CIRCUIT

Halyani binti Mohd Yassim

halyani@utem.edu.my

LESSON OUTCOME


At the end of this chapter, students are able:



to describe second order
source-free series RLC circuit

SUBTOPICS


Introduction of
Second Order
Circuit




Source-free
Series RLC Circuit




INTRODUCTION

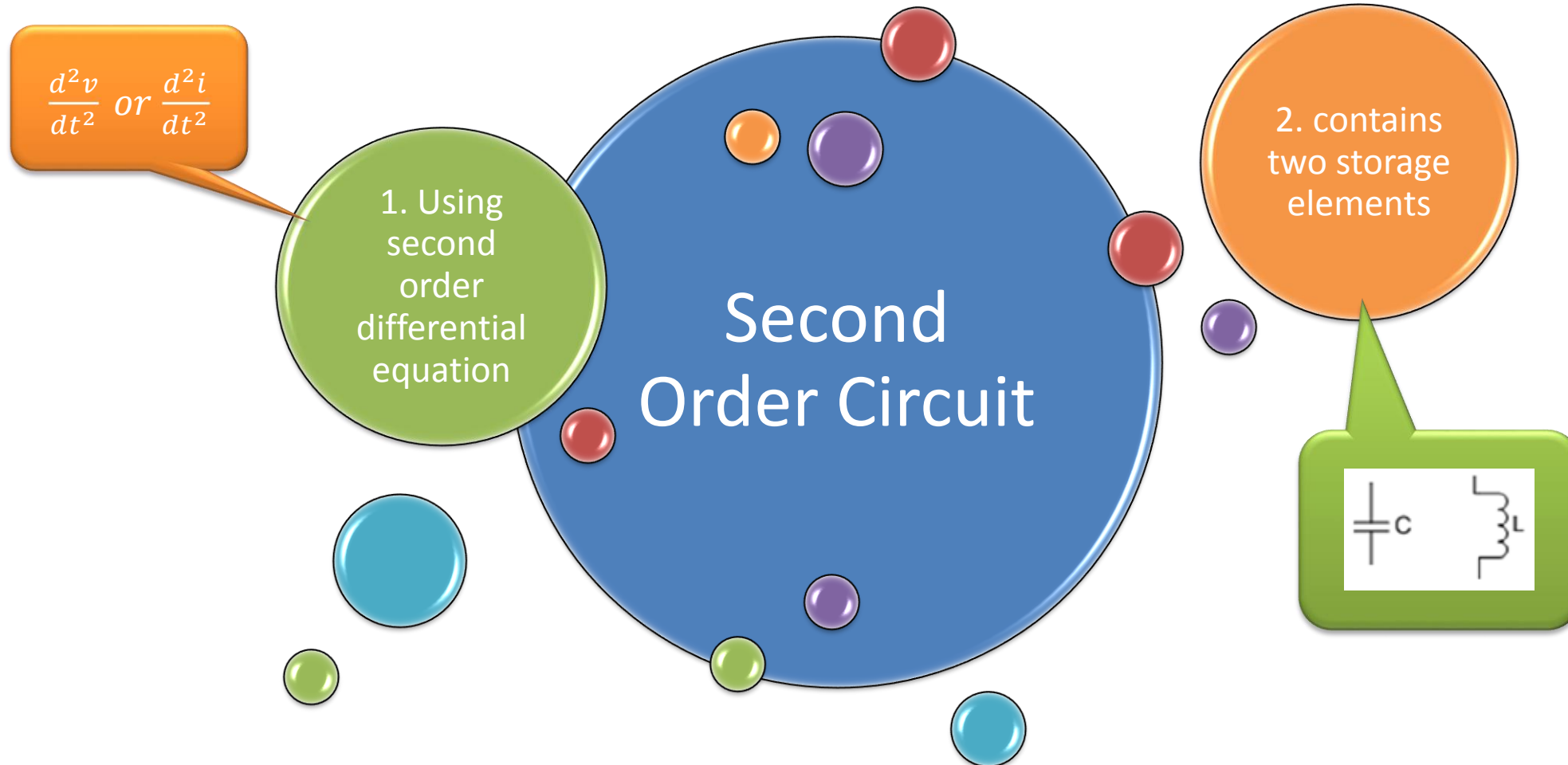

INTRODUCTION

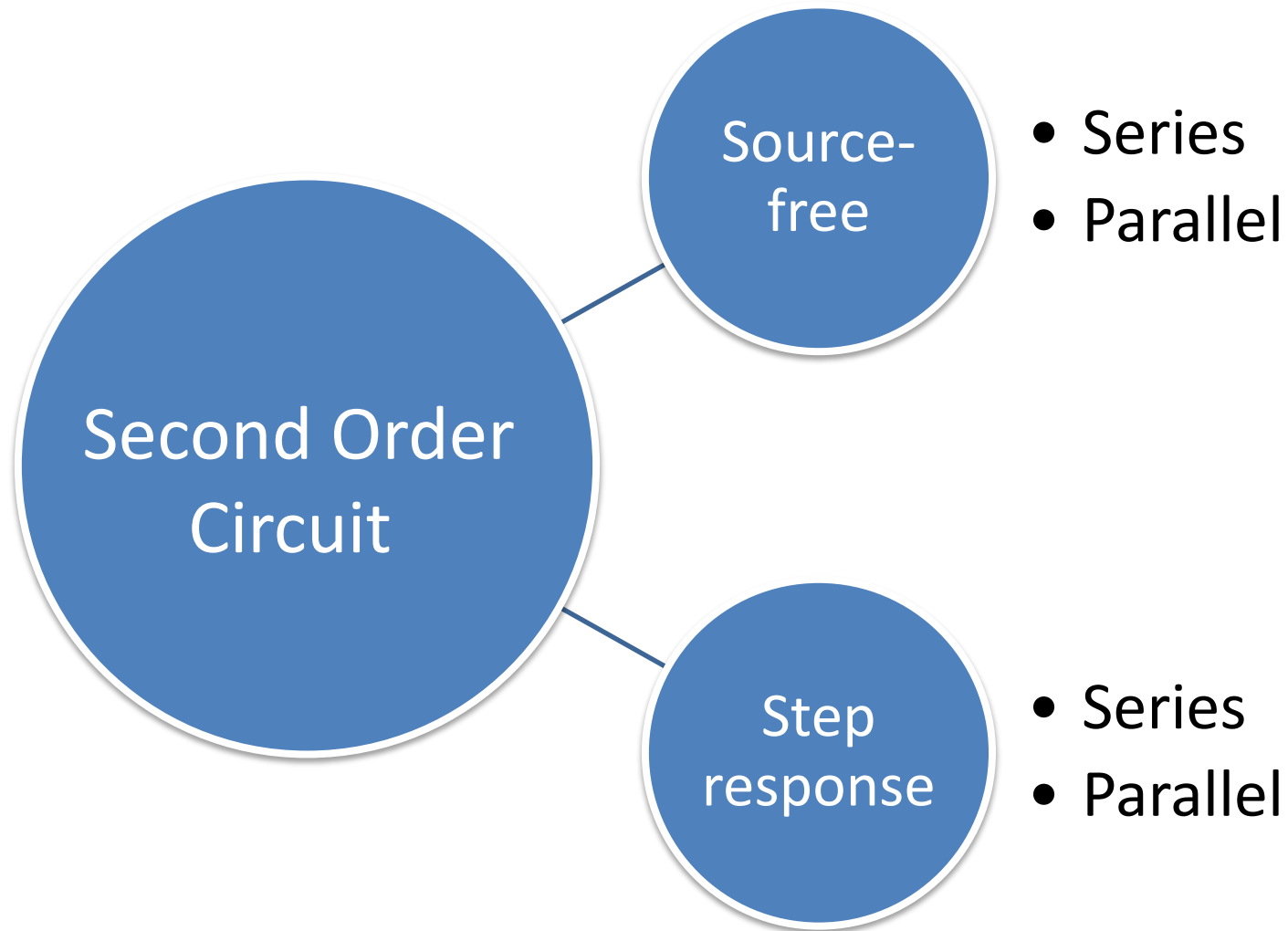

SOURCE-FREE SERIES RLC CIRCUIT

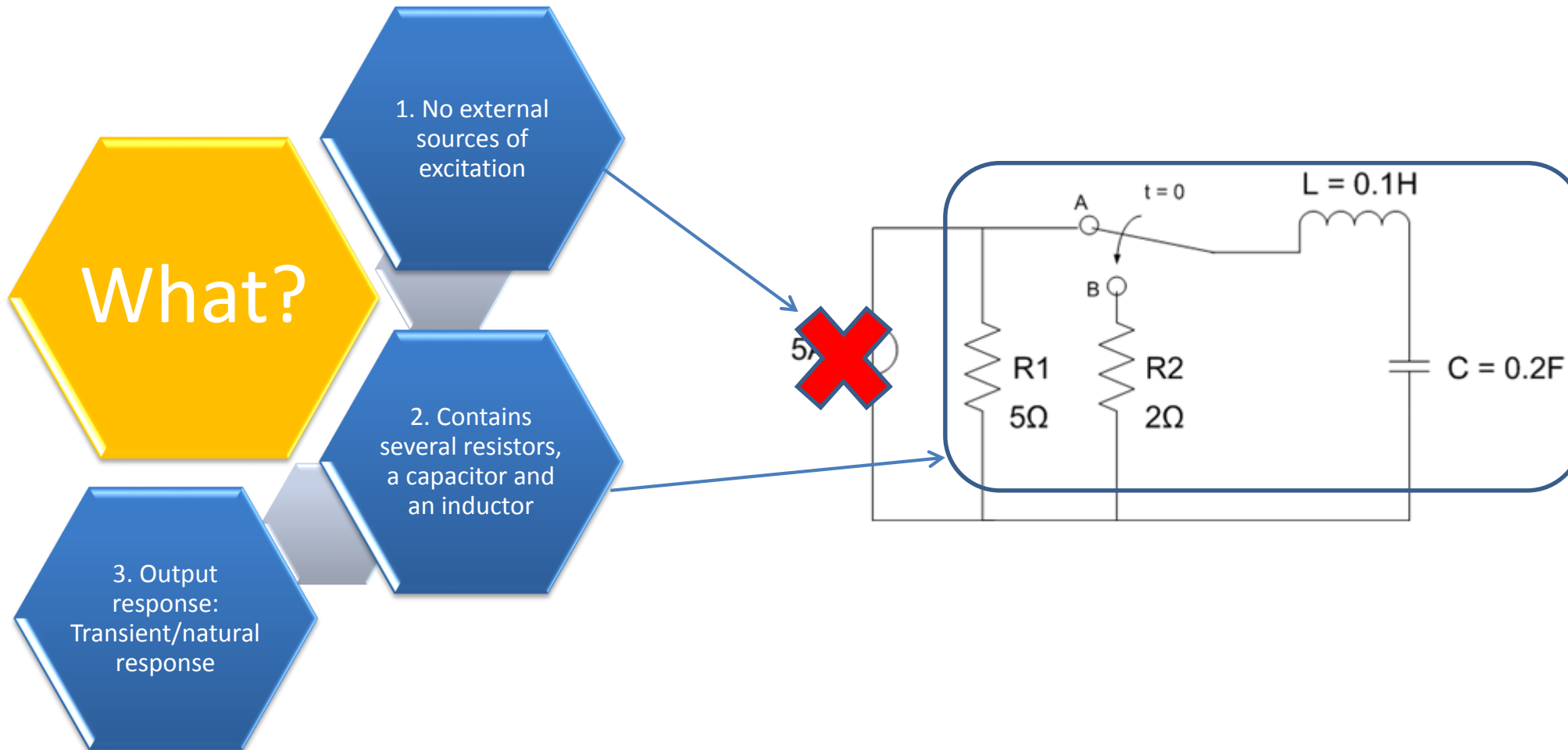

SOURCE-FREE SERIES RLC CIRCUIT

Source-free Series RLC Circuit

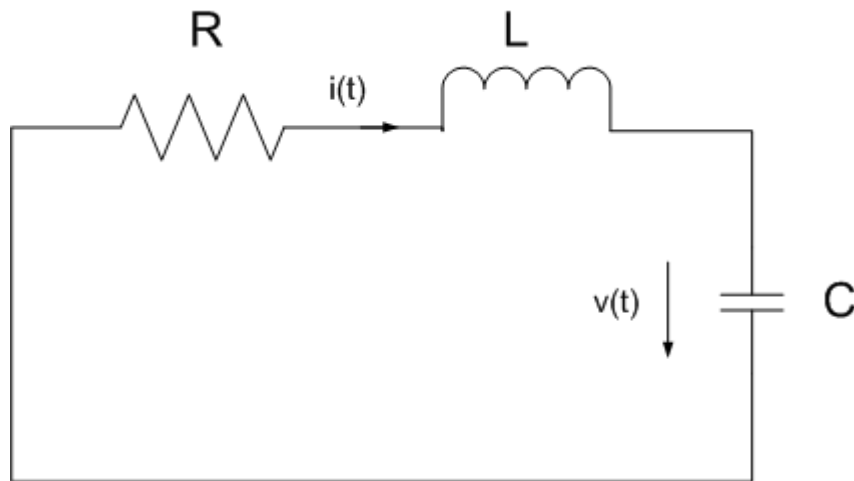


Figure 1

Assumption:

$$i(0) = I_0 \quad \text{and} \quad v(0) = \frac{1}{C} \int_{-\infty}^0 i(t) dt = V_0$$

Initial current
through inductor

Initial voltage
across
capacitor

By Applying Kirchhoff's Voltage Law:

$$V_R + V_L + V_C = 0$$

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^0 i(t) dt = 0$$

Second order differential equation:

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

SOURCE-FREE SERIES RLC CIRCUIT

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Roots of the characteristic equation

$$\alpha = \frac{R}{2L},$$

Damping factor

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Undamped natural frequency

Types of natural response of source-free series RLC circuit:

1. Overdamped response ($\alpha > \omega_0$)

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$
2. Critically damped response ($\alpha = \omega_0$)

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$
3. Underdamped response ($\alpha < \omega_0$)

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

Note: A_1 and A_2 can be determined from the initial conditions namely $i(0)$ and $\frac{di(0)}{dt}$.

$$\frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0)$$

EXAMPLE 1

The switch in Figure 2 moves from position A to B at $t = 0$. Find $i(t)$ for $t > 0$.

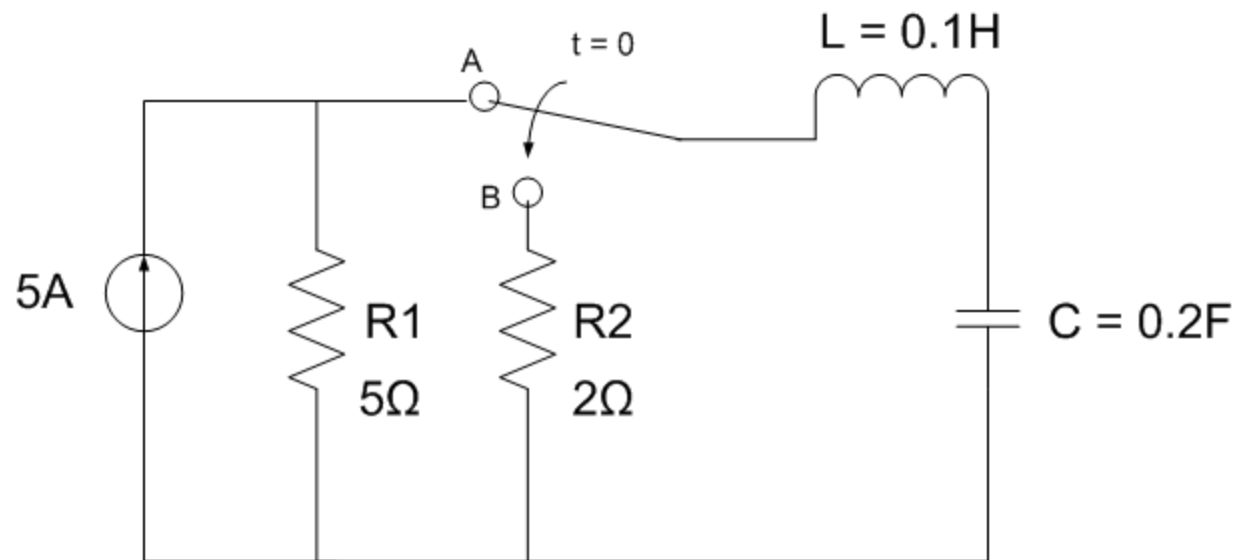


Figure 2

SOLUTION 1

Step 1: Find initial voltage across capacitor, V_0 and initial current through inductor, I_0 when $t < 0$.

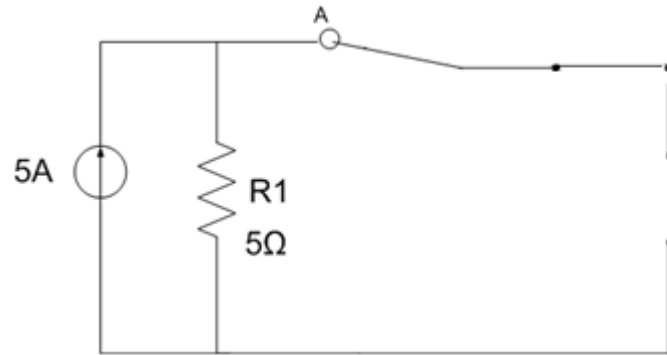


Figure 3

Tips 1:

When $t < 0$, capacitor acts like an open circuit and inductor acts like a short circuit.

Tips 2:

There is no current flow through inductor due to open circuit.

$$i(0) = 0A$$

$$v(0) = iR = 5A * 5\Omega = 25V$$

SOLUTION 1

Step 2: Determine type of natural response of this circuit when $t > 0$.

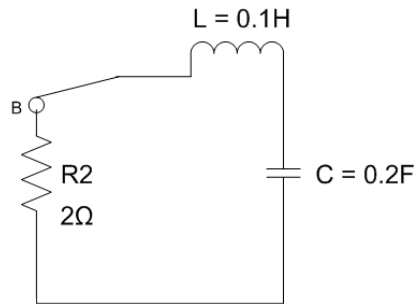


Figure 4

$$\alpha = \frac{R}{2L} = \frac{2}{2 * 0.1} = 10, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 * 0.2}} = 7.071$$

$\alpha > \omega_0 \rightarrow$ overdamped response

Current response for overdamped case:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

SOLUTION 1

Step 3: Find roots of characteristic equation for this circuit.

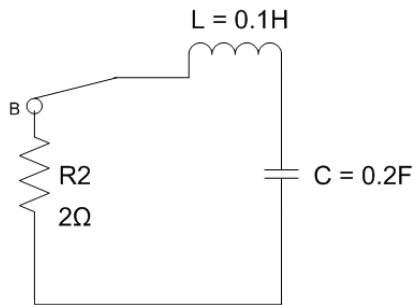


Figure 5

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\frac{2}{2 * 0.1} \pm \sqrt{\left(\frac{2}{2 * 0.1}\right)^2 - \frac{1}{0.1 * 0.2}}$$

$$s_{1,2} = -0.36, \quad -19.64$$

SOLUTION 1

Step 4: Determine A_1 and A_2 from initial conditions

$i(0)$ and $\frac{di(0)}{dt}$, when $t > 0$.

$$i(0) = A_1 e^{-0.36(0)} + A_2 e^{-19.64(0)} = 0A$$

$$A_1 + A_2 = 0 \rightarrow A_1 = -A_2$$

$$\frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0) = -\frac{1}{0.1}(2(0) + 25) = -250 \frac{A}{s}$$

$$\frac{di}{dt} = -0.36 * A_1 e^{-0.36t} - 19.64 * A_2 e^{-19.64t}$$

$$\frac{di(0)}{dt} = -0.36 * A_1 e^{-0.36(0)} - 19.64 * A_2 e^{-19.64(0)} = -250$$

$$0.36 * A_2 - 19.64 * A_2 = -250 \rightarrow A_2 = 13$$

$$\rightarrow A_1 = -13$$

Current response:

$$i(t) = -13e^{-0.36t} + 13e^{-19.64t} A$$

EXAMPLE 2

Calculate $i(t)$ for $t > 0$ in the circuit of Figure 6.

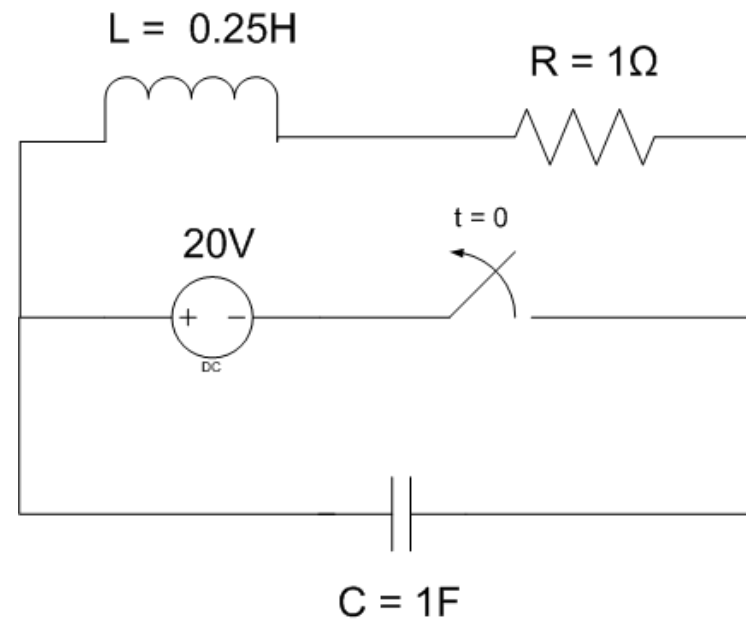


Figure 6

SOLUTION 2

Step 1: Find initial voltage across capacitor, V_0 and initial current through inductor, I_0 when $t < 0$.

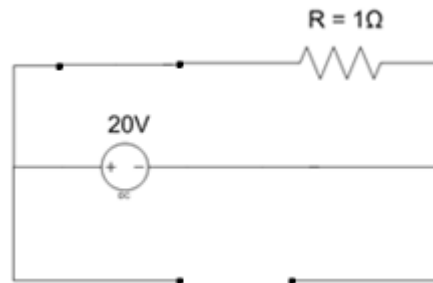


Figure 7

Tips 1:

When $t < 0$, capacitor acts like an open circuit and inductor acts like a short circuit.

Tips 2:

Current flows through inductor, which is less resistance than capacitor.

$$V_0 = 20V$$

$$I_0 = \frac{V}{R} = \frac{20V}{1\Omega} = 20A$$

SOLUTION 2

Step 2: Determine type of natural response of this circuit when $t > 0$.

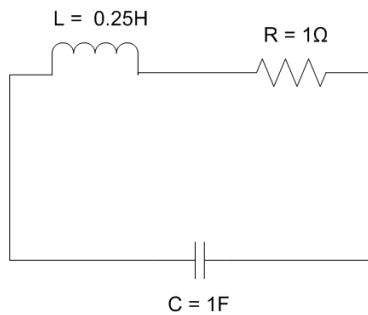


Figure 8

$$\alpha = \frac{R}{2L} = \frac{1}{2 * 0.25} = 2, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.25 * 1}} = 2$$

$\alpha = \omega_0 \rightarrow$ critically damped response

Current response for critically damped case:

$$i(t) = (A_2 + A_1 t)e^{-\alpha t}$$

SOLUTION 2

Step 3: Determine A_1 and A_2 from initial conditions

$i(0)$ and $\frac{di(0)}{dt}$, when $t > 0$.

$$i(0) = (A_2 + A_1(0))e^{-2(0)} = 20A, \quad \rightarrow A_2 = 2$$

$$\frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0) = -\frac{1}{0.25}(1(20) + 20) = -160 \frac{A}{s}$$

$$\frac{di}{dt} = -2(A_2 + A_1t)e^{-2t} + A_1e^{-2t}$$

$$\begin{aligned} \frac{di(0)}{dt} &= -2(2 + A_1(0))e^{-2(0)} + A_1e^{-2(0)} = -160 \\ -4 + A_1 &= -160 \rightarrow A_1 = -156 \end{aligned}$$

Current response:

$$i(t) = (2 - 156t)e^{-2t} A$$

SELF REVIEW QUESTIONS

1. A source-free RL circuit is an example of second order circuit.

☐ TRUE

☐ FALSE

2. Name two storage elements in a second order source-free RLC circuit.

Answer: _____

3. Given $R = 10\Omega$ and $C = 0.5F$. Determine the value of L so that the natural response of source-free series RLC circuit is critically damped response.

a) 1.25H

b) 12.5H

c) 125H

d) 0.125H

4. Following is TRUE about a second order circuit except

a) consists of a resistor and two capacitors in a circuit

b) is described using second order differential equation

c) consists of one storage elements

d) has three types of natural response

5. Given $L = 2H$ and $C = 4F$. Interpret the value of R when $\alpha > \omega_0$.

a) $R > 2$

b) $R < 0.5$

c) $R > 0.2$

d) $R < 5$

ANSWERS

1. FALSE
2. Inductor and capacitor
3. b
4. c
5. a