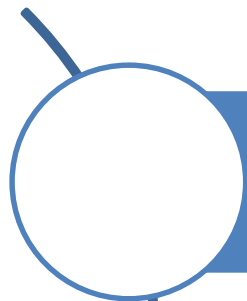


# ADVANCED ELECTRICAL CIRCUIT BETI 1333 FIRST ORDER SOURCE-FREE RC AND RL CIRCUIT


Halyani binti Mohd Yassim<sup>1</sup>, Nurul Ashikin binti Mohd Rais<sup>2</sup>,  
[1halyani@utem.edu.my](mailto:halyani@utem.edu.my), [2nurulashikin@utem.edu.my](mailto:nurulashikin@utem.edu.my),
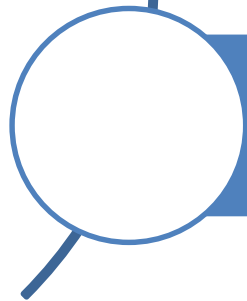
# LESSON OUTCOMES

At the end of this chapter, students are able:



to describe first order source-free RC and RL circuit



to illustrate output response of first order source-free RC and RL circuit

# SUBTOPICS


Source-free RC  
Circuit



Source-free RL  
Circuit



# INTRODUCTION

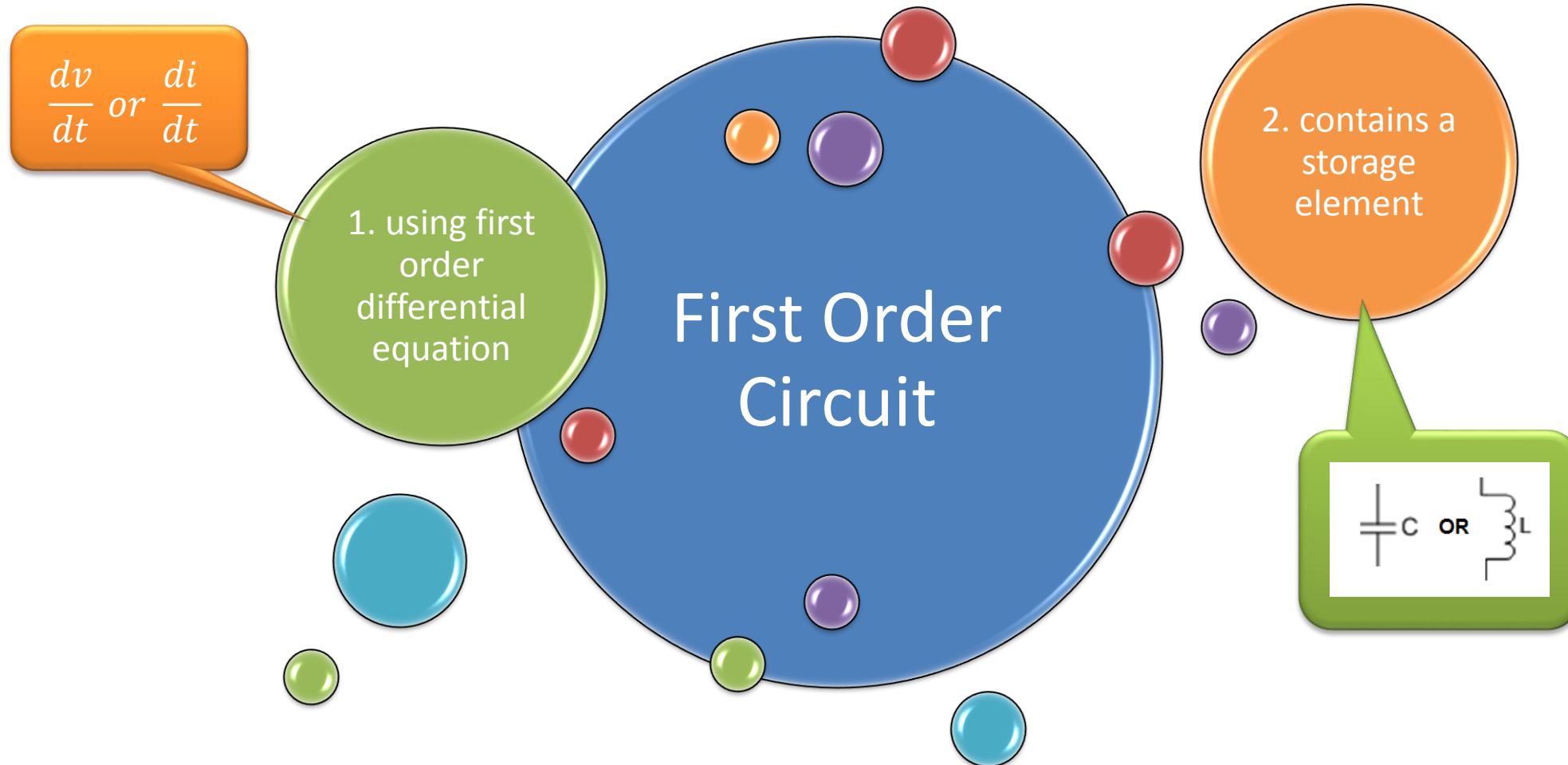



# SOURCE-FREE RC CIRCUIT

What?

1. No external sources of excitation

2. Contains several resistors and a capacitor

3. Output response = Natural response

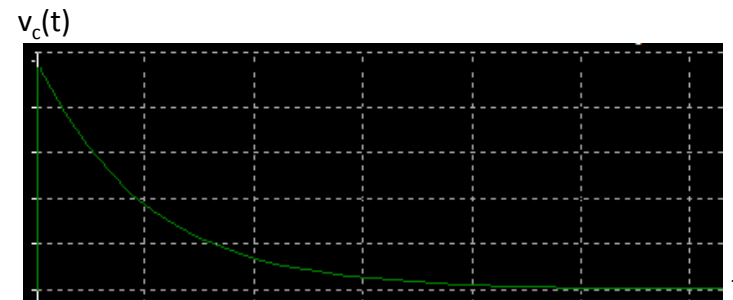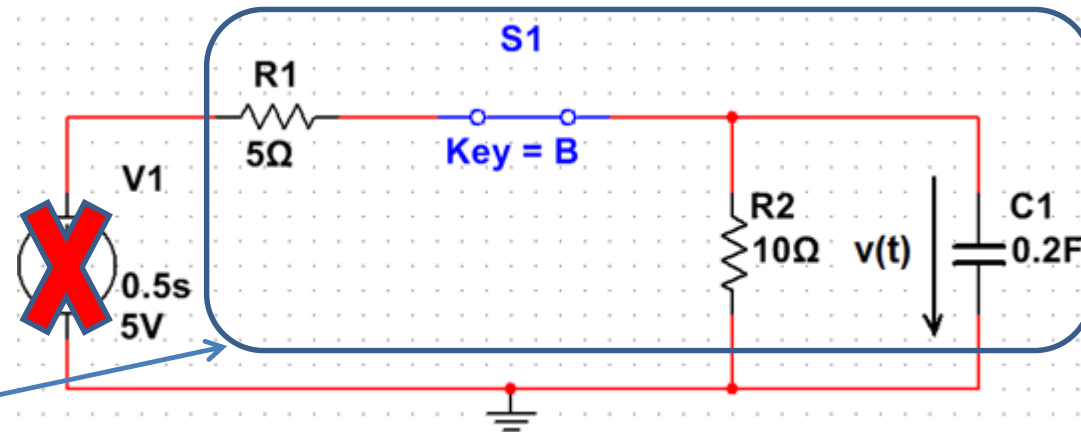

# SOURCE-FREE RC CIRCUIT

SERIES RC CIRCUIT

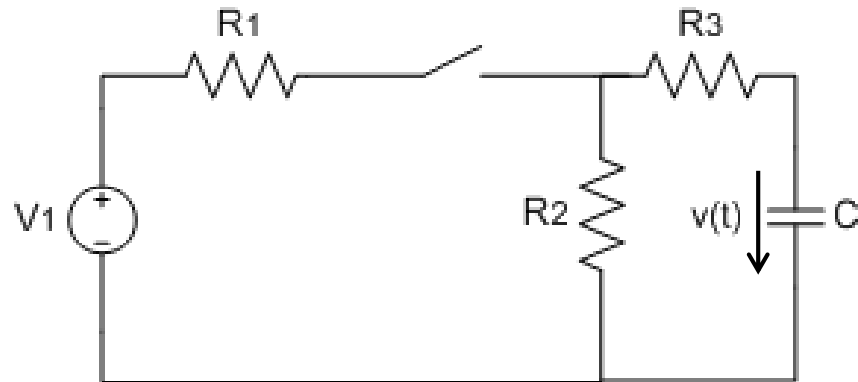


Figure 1

PARALLEL RC CIRCUIT

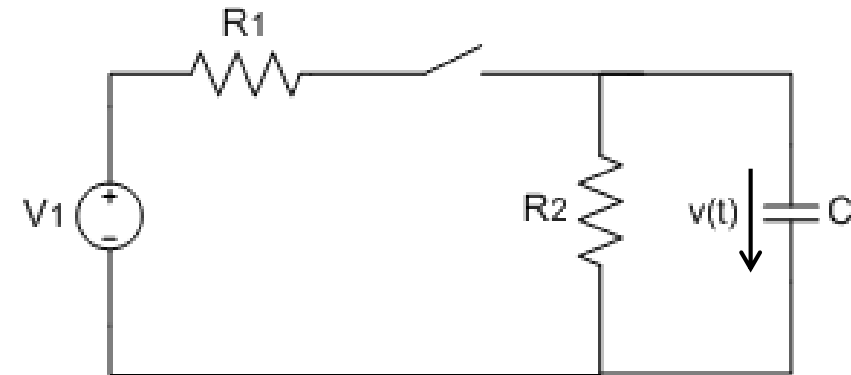


Figure 2

# SOURCE-FREE RC CIRCUIT

## Source-free RC Circuit:

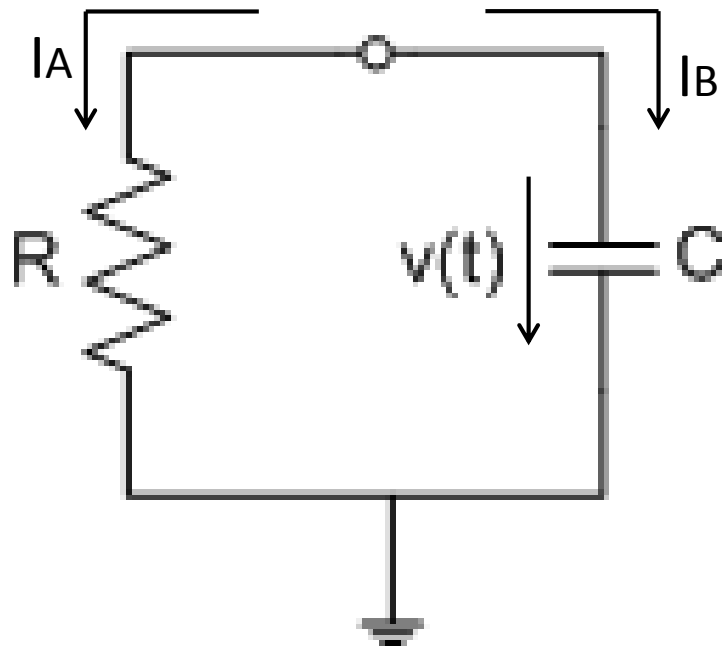


Figure 3

## By applying Kirchhoff's Current Law:

$$I_A + I_B = 0$$

$$\frac{v}{R} + C \frac{dv}{dt} = 0$$

Ohm's Law

Capacitor Law

## Output response:

$$v(t) = V_0 e^{-t/\tau}$$

Time constant  
 $\tau = RC$

Initial voltage  
across Capacitor

# EXAMPLE 1

The switch in Figure 1 is opened at  $t = 0$ . Find  $v(t)$  for  $t \geq 0$ .

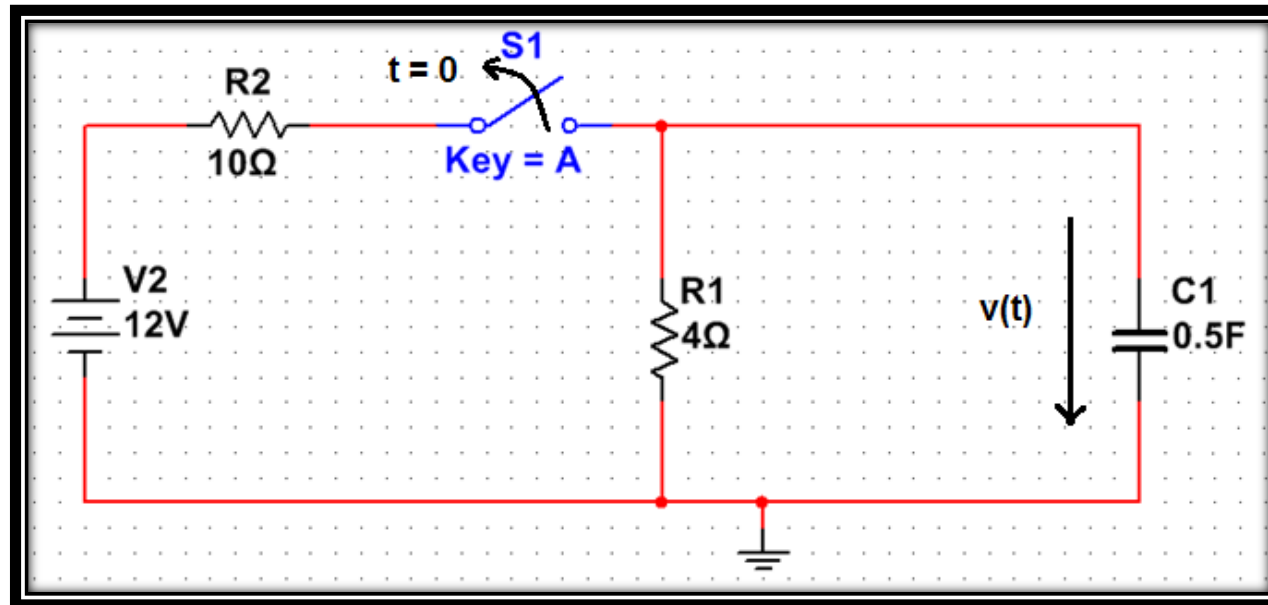


Figure 4



# SOLUTION 1

**Step 1:** Find initial voltage across capacitor,  $V_0$  when  $t < 0$ .

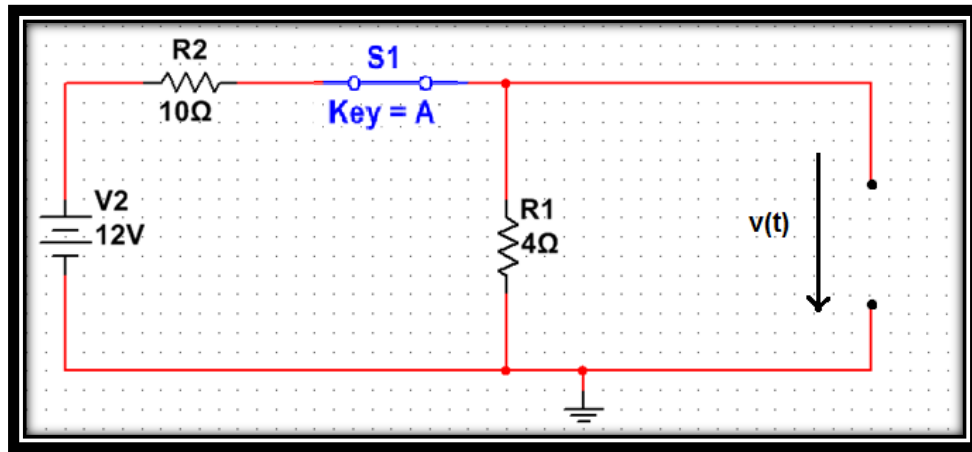


Figure 5

$$v(t) = V_0 = \frac{R_1}{R_1 + R_2} V_2 = \frac{4\Omega}{(4 + 10)\Omega} = 2V$$

**Tips 1:**

Initially, capacitor is not charged. When  $t < 0$ , it acts like an open circuit.

**Tips 2:**

$$v(0^-) = v(0)$$

# SOLUTION 1

**Step 2:** Find time constant,  $\tau$  for  $t \geq 0$ .

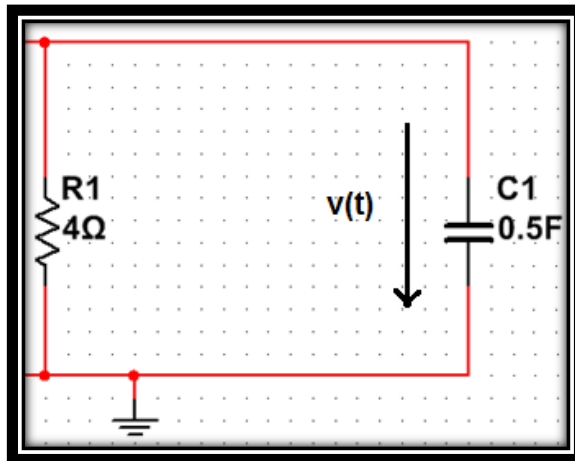


Figure 6

$$\tau = R_1 C = 4\Omega * 0.5F = 2s$$

**Tips 3:**

When  $t \geq 0$ , circuit in Figure 4 is reduced to Figure 6.

# SOLUTION 1

**Step 3:** Find voltage across capacitor,  $v(t)$  for  $t \geq 0$ .

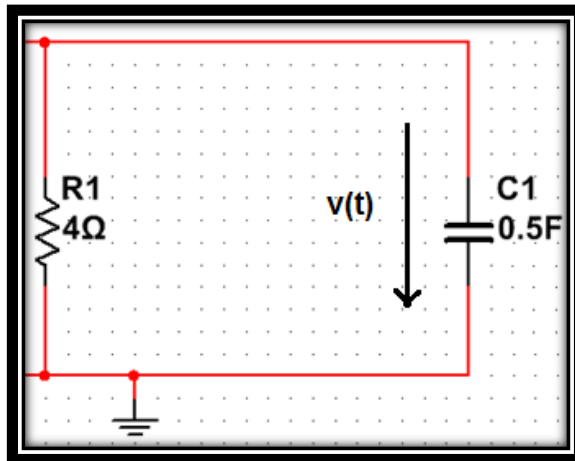


Figure 7


$$v(t) = V_0 e^{-t/\tau} = 2e^{-0.5t} \text{V}$$

# OUTPUT RESPONSE 1

Natural response of an RC circuit in Figure 4:


V(1): Voltage across capacitor

V(2): Voltage source

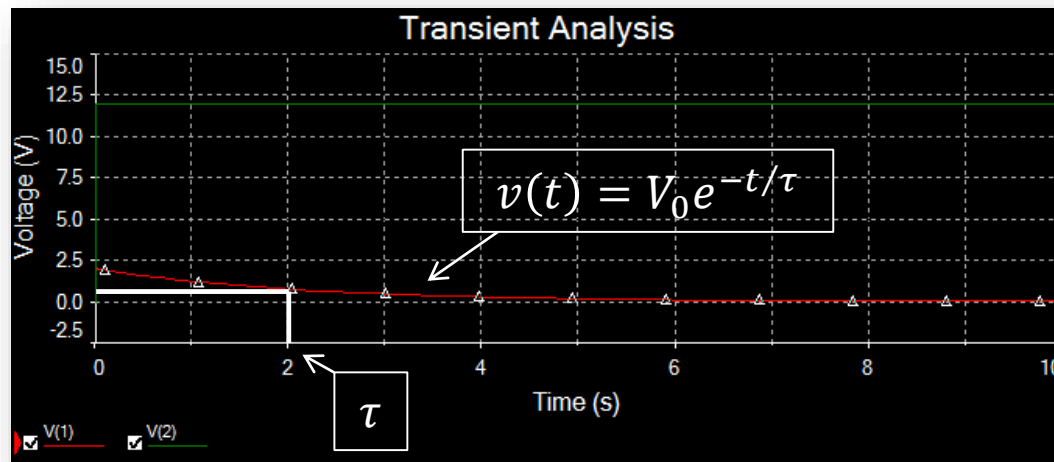

Graph 1

# SOURCE-FREE RL CIRCUIT

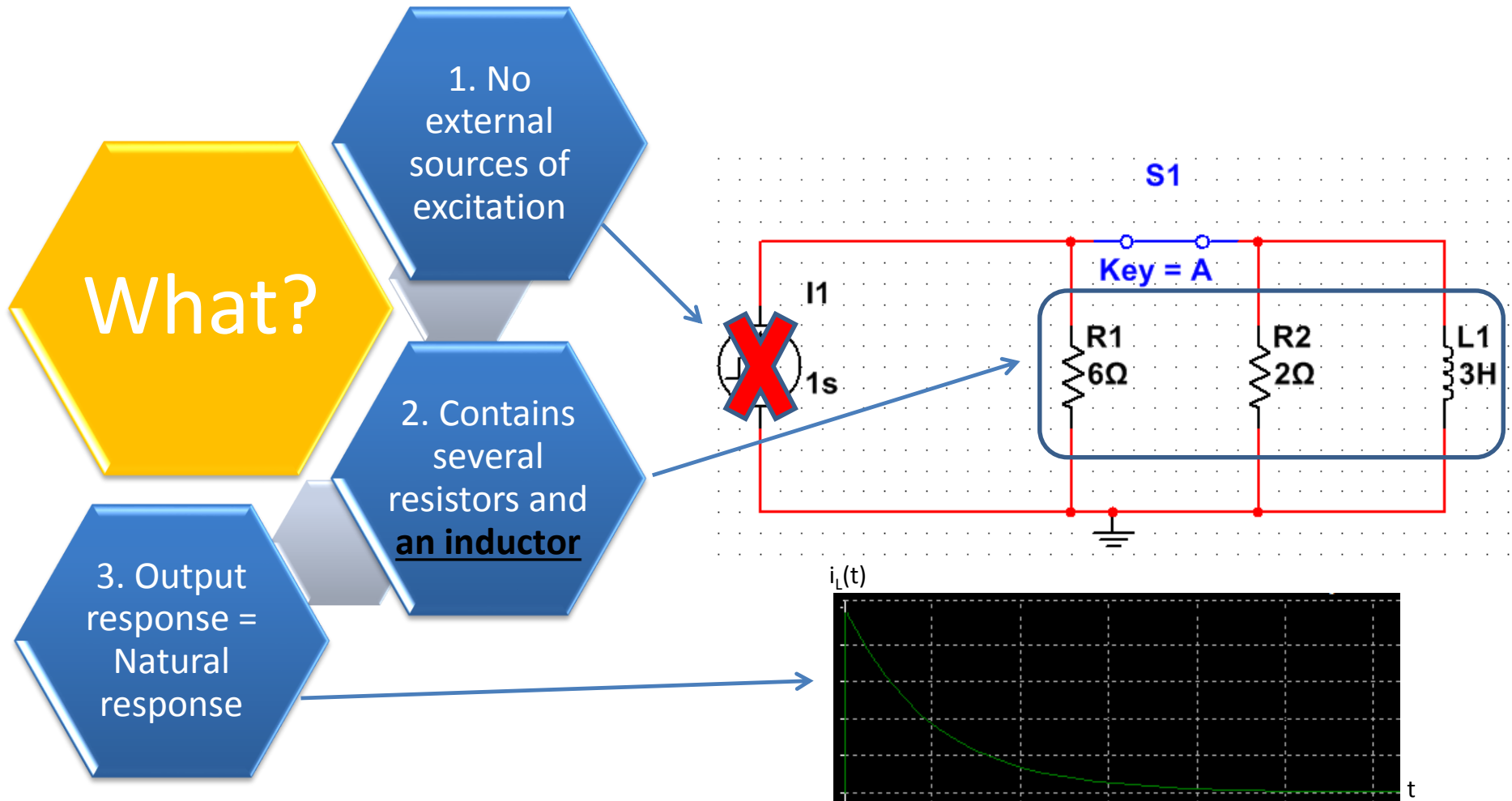

# SOURCE-FREE RL CIRCUIT

SERIES RL CIRCUIT

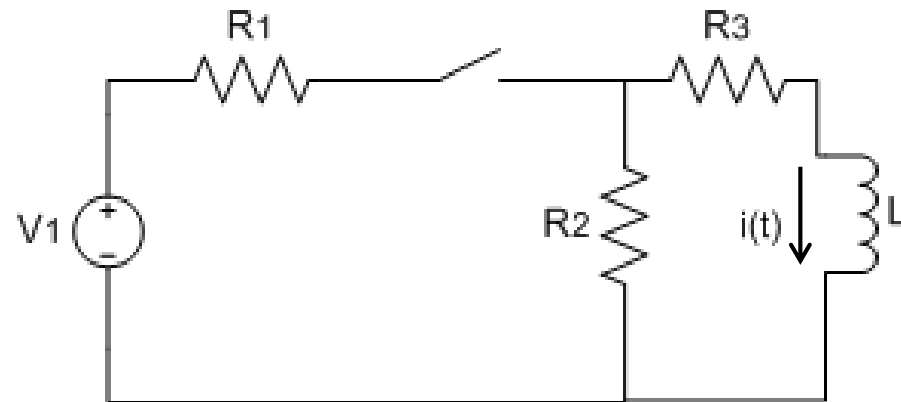


Figure 8

PARALLEL RL CIRCUIT

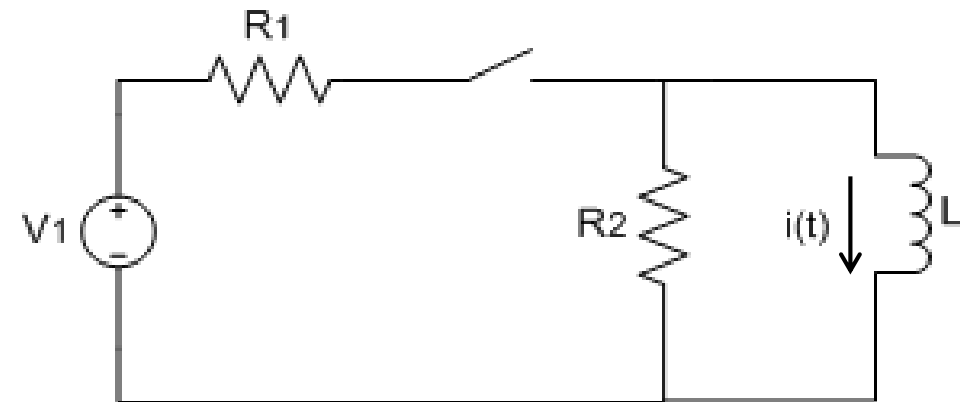


Figure 9

# SOURCE-FREE RL CIRCUIT

## Source-free RL Circuit:

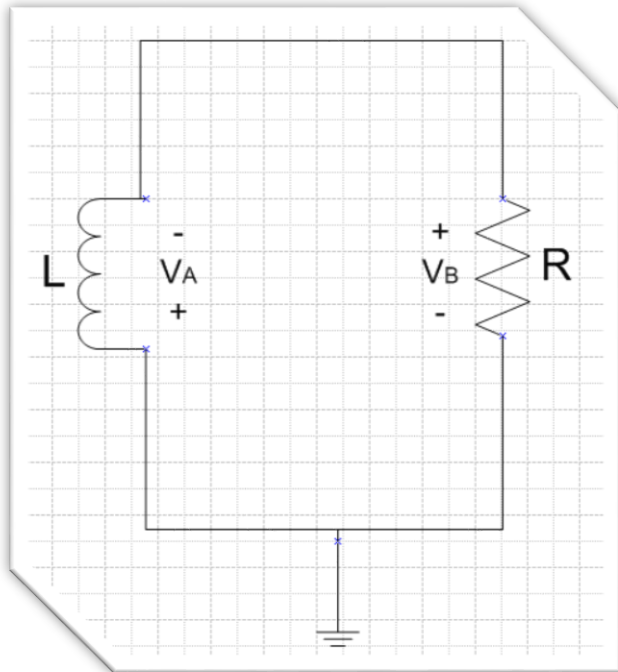


Figure 10

## By applying Kirchhoff's Voltage Law:

$$V_A + V_B = 0$$

$$L \frac{di}{dt} + iR = 0$$

Ohm's Law

Inductor Law

## Output response:

$$i(t) = I_0 e^{-t/\tau}$$

Time constant

$$\tau = \frac{L}{R}$$

Initial current  
through inductor

# EXAMPLE 2

The switch in Figure 11 is opened for  $t = 0$ . Find  $i(t)$  for  $t > 0$ .

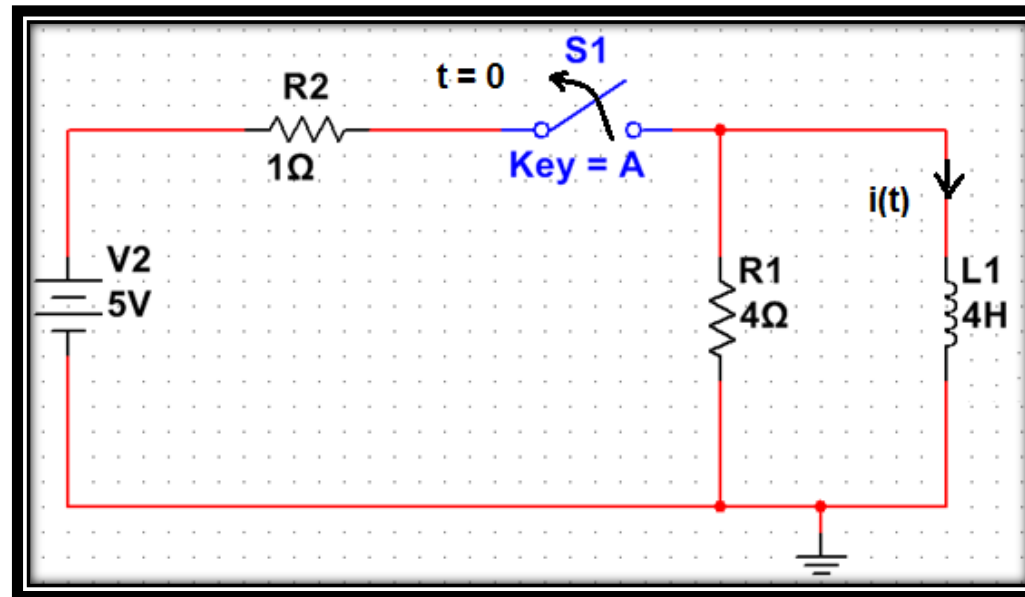


Figure 11



# SOLUTION 2

**Step 1:** Find initial current through inductor,  $I_0$  when  $t < 0$ .

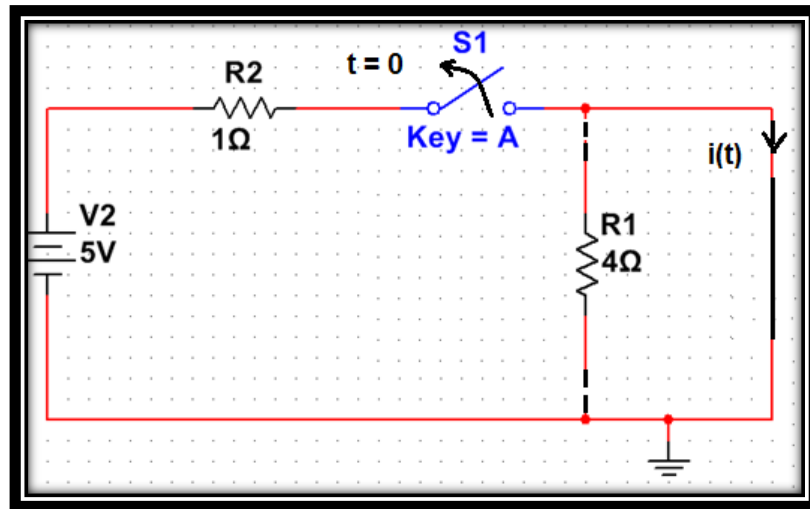


Figure 12

$$i(t) = I_0 = \frac{V_2}{R} = \frac{5V}{1\Omega} = 5A$$

## Tips 1:

Initially, inductor is not charged. When  $t < 0$ , it acts like a short circuit.

## Tips 2:

Current will flow to the less resistance.

## Tips 3:

$$i(0^-) = i(0)$$

# SOLUTION 2

**Step 2:** Find time constant,  $\tau$  for  $t > 0$ .

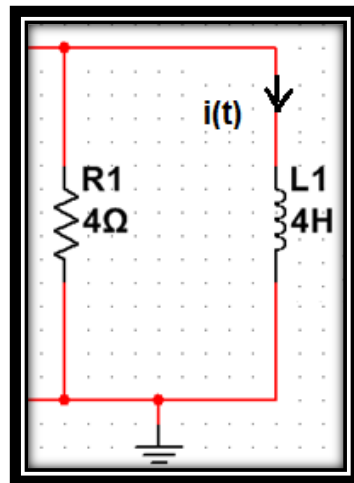


Figure 13

**Tips 4:**

When  $t > 0$ , circuit in Figure 11 is reduced to Figure 13.

$$\tau = \frac{L}{R_1} = \frac{4H}{4\Omega} = 1s$$

# SOLUTION 2

**Step 3:** Find current through inductor,  $i(t)$  for  $t > 0$ .

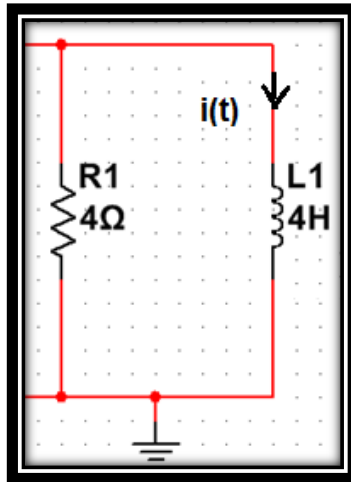


Figure 14


$$i(t) = I_0 e^{-t/\tau} = 5e^{-t} A$$

# OUTPUT RESPONSE 2

Natural response of an RL circuit in Figure 11:

I(L1): Current across inductor

V(2): Voltage source

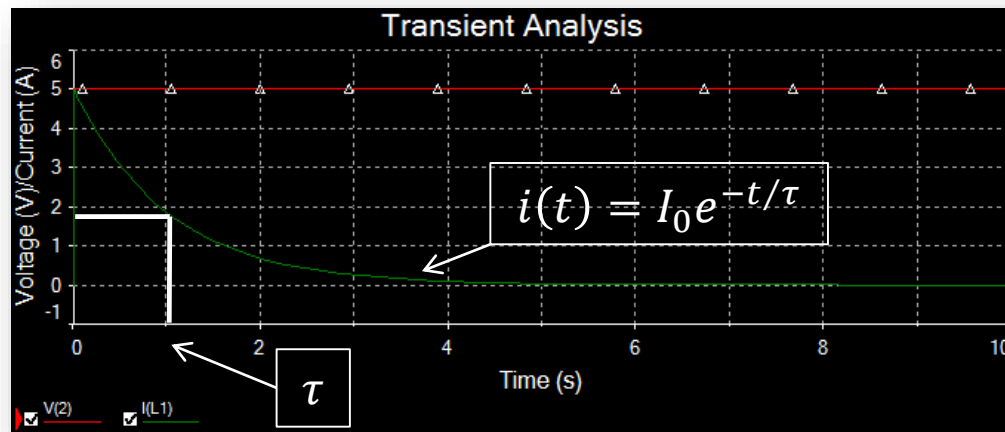

Graph 2

# SELF REVIEW QUESTIONS

1. A source-free circuit has no external sources of excitation.

☐ TRUE

☐ FALSE

2. Name a storage element in a first order source-free RC circuit.

Answer: \_\_\_\_\_

3. Forced response is the behavior of a first order source-free circuit.

☐ TRUE

☐ FALSE

4. Given  $R = 4 \Omega$  and  $C = 5 \text{ F}$ . What is the time constant for this RC circuit?

a) 1 s

b) 3 s

c) 10 s

d) 20 s

5. An inductor in a source-free RL circuit with  $L = 2 \text{ H}$  and  $R = 10 \Omega$  is being charged. What is the time required for the inductor current to decay 50 % of its initial value?

a) 0.20 s

b) 0.05 s

c) 0.14 s

d) 0.35 s

# ANSWERS

1. TRUE
2. Capacitor
3. FALSE
4. d
5. c