



UTeM

UNIVERSITI TEKNIKAL MALAYSIA MELAKA

OPENCOURSEWARE

ADVANCED ELECTRICAL CIRCUIT

BETI 1333

FIRST ORDER STEP RESPONSE RC CIRCUIT

Nurul Ashikin binti Mohd Rais


nurulashikin@utem.edu.my




ocw.utem.edu.my

LESSON OUTCOMES

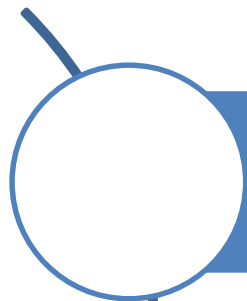At the end of this chapter, students are able:



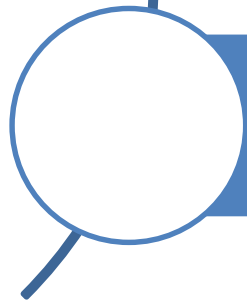to describe first order step response RC circuit




to illustrate output response of first order step response RC circuit

SUBTOPICS

Singularity
Functions

Step response RC
Circuit

SINGULARITY FUNCTIONS

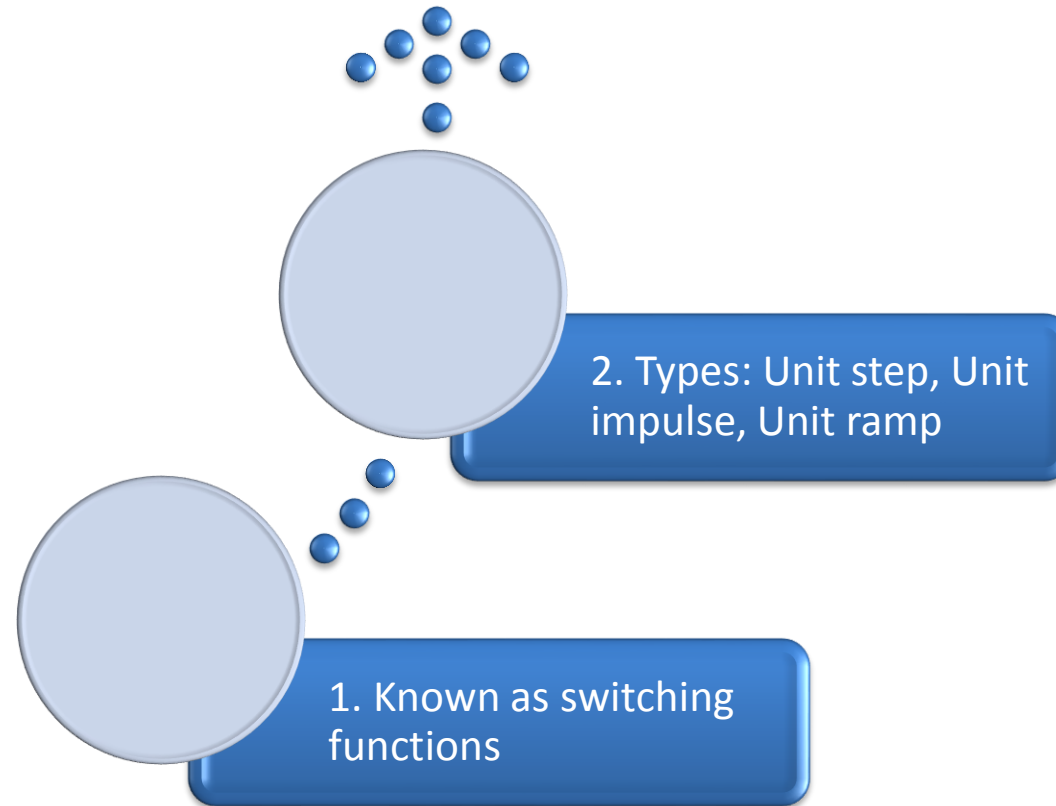

SINGULARITY FUNCTIONS

Voltage Source

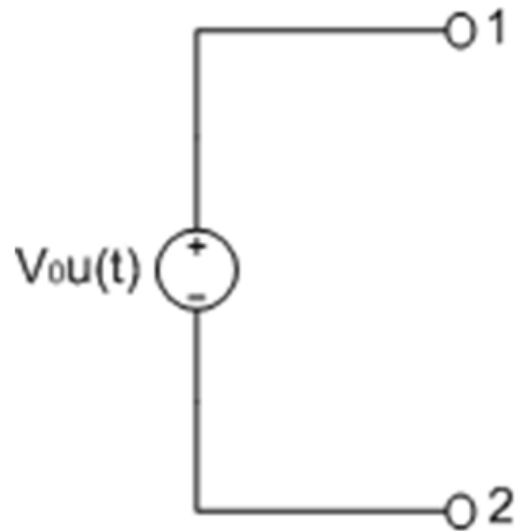


Figure 1

=

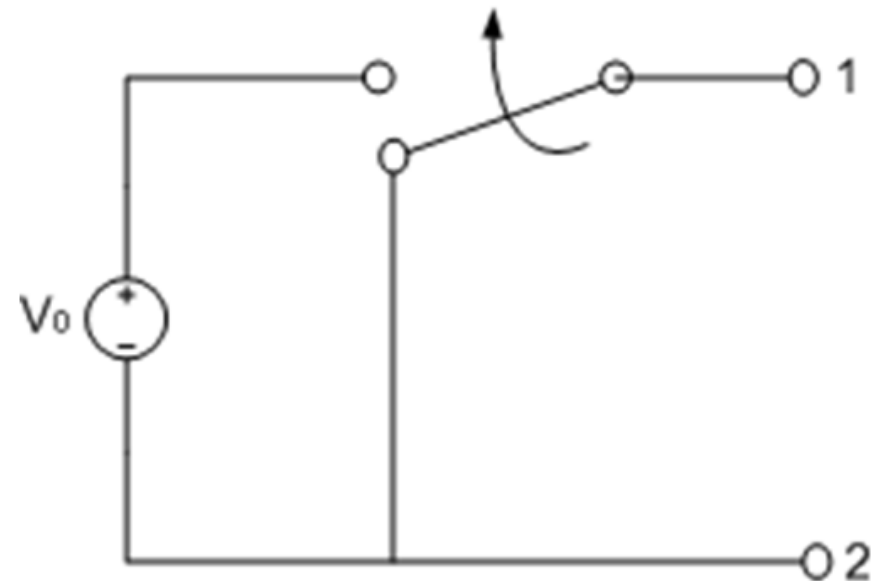


Figure 2

SINGULARITY FUNCTIONS

Current Source

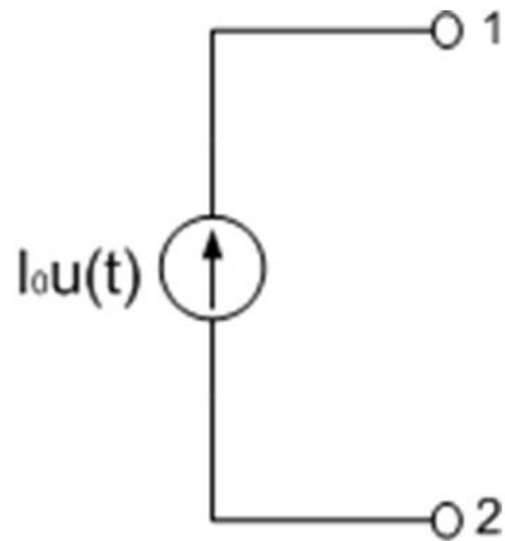


Figure 3

=


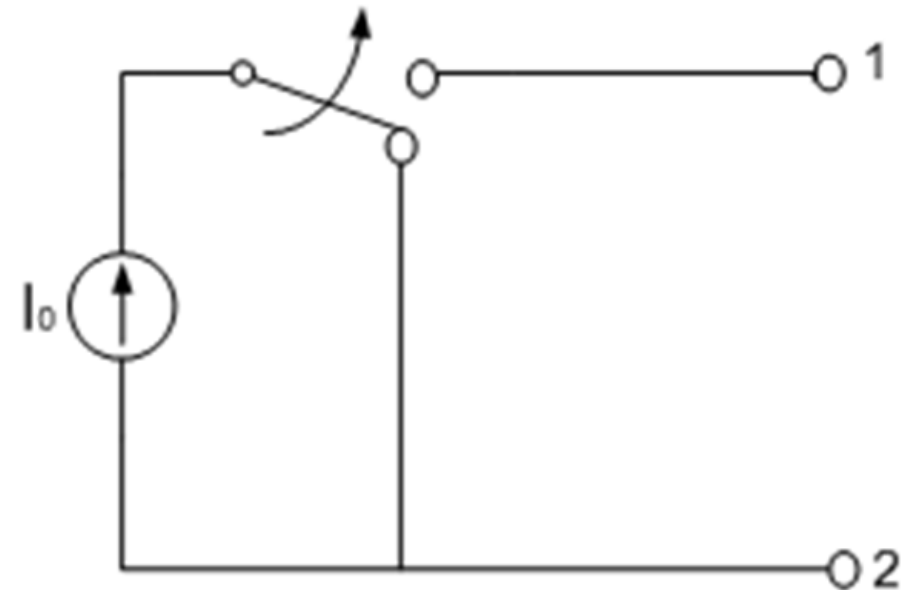


Figure 4

SINGULARITY FUNCTIONS

Unit Step Function:

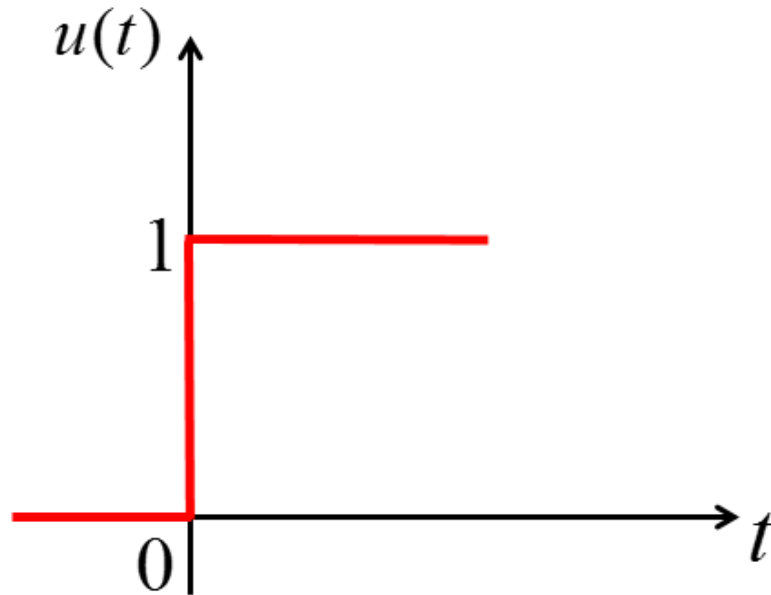

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

Figure 5

SINGULARITY FUNCTIONS

Unit Impulse Function:

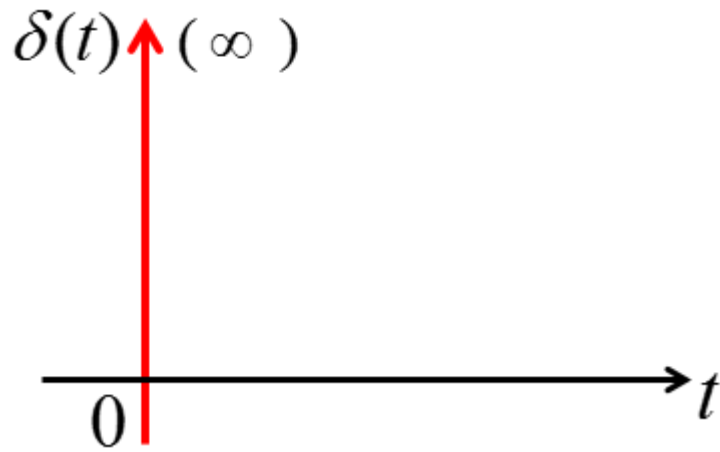


Figure 6

$$\delta(t) = \frac{d}{dt}u(t) = \begin{cases} 0, & t < 0 \\ Undefined, & t = 0 \\ 0, & t > 0 \end{cases}$$

SINGULARITY FUNCTIONS

Unit Ramp Function:


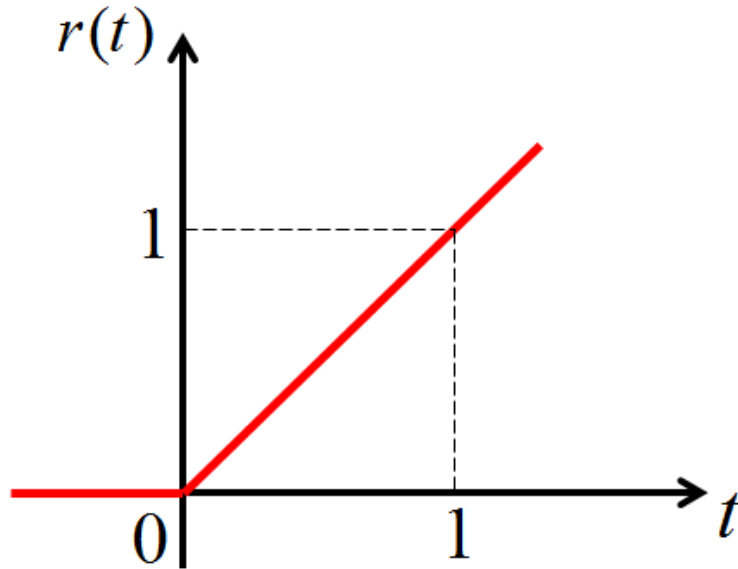


Figure 7

$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$

STEP RESPONSE RC CIRCUIT

W
H
A
T
?

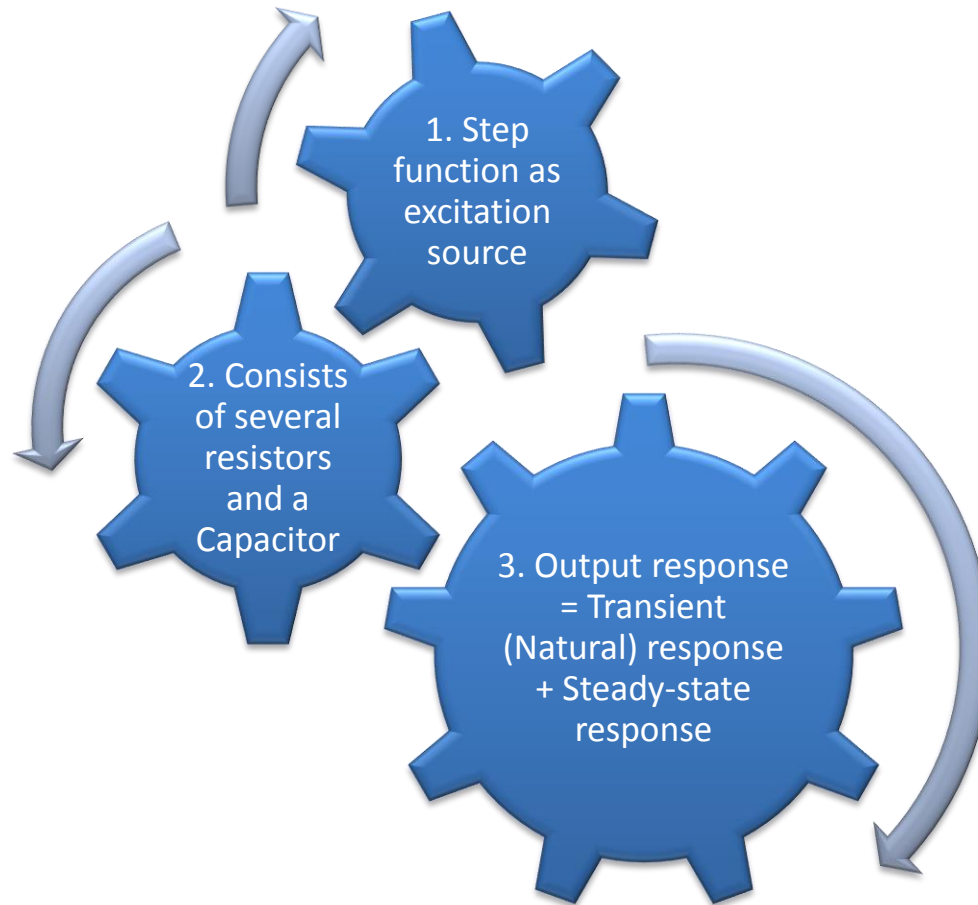

STEP RESPONSE RC CIRCUIT

SERIES RC CIRCUIT

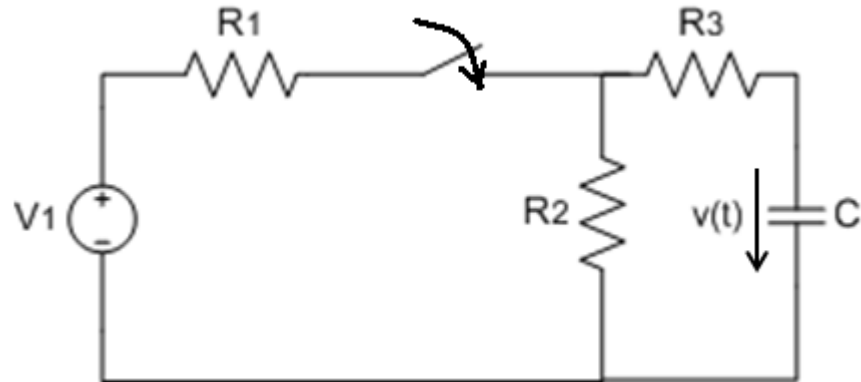


Figure 8

PARALLEL RC CIRCUIT

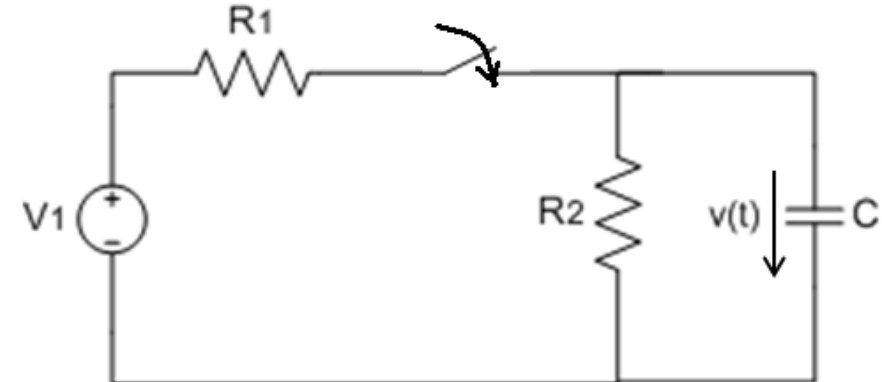


Figure 9

STEP RESPONSE RC CIRCUIT

RC Circuit:

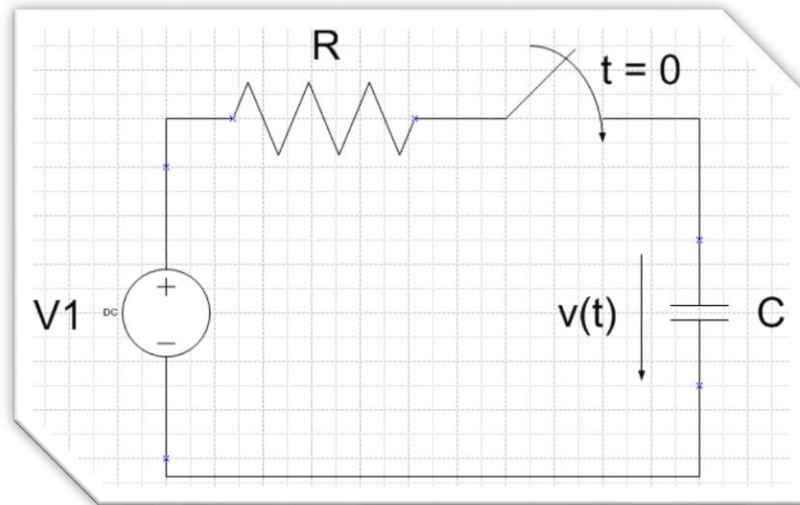


Figure 10

Output response:

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

Final voltage
across capacitor,
when $t = \infty$

Initial voltage
across capacitor,
when $t = 0$

Time constant
($\tau = RC$)

EXAMPLE 1

The switch in Figure 11 is closed at $t = 0.5$ s. Find $v(t)$ for $t > 0.5$ s.

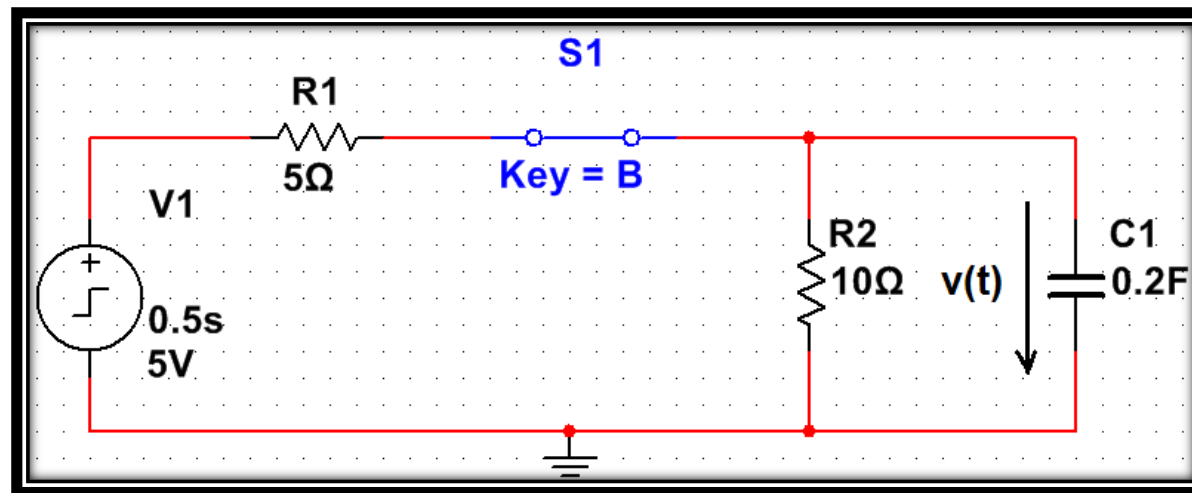


Figure 11

SOLUTION 1

Step 1: Find initial voltage across capacitor when $t < 0.5$ s. Below is the circuit when switch is opened for $t < 0.5$ s.

Tips 1:

When $t < 0.5$ s, capacitor acts like an open circuit.

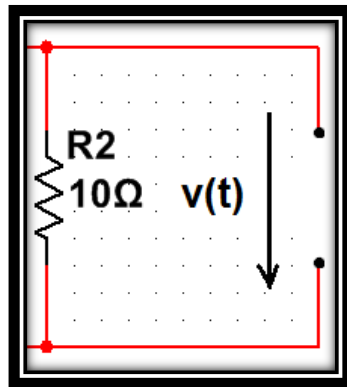


Figure 12

$$v(t) = v(0.5) = 0 \text{ V}$$

SOLUTION 1

Step 2: Find time constant, τ for $t > 0.5$ s.

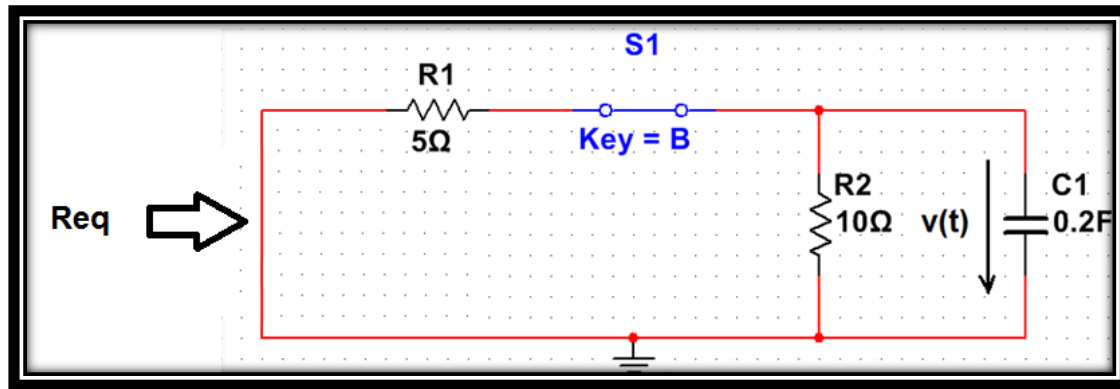


Figure 13

$$R_{eq} = \frac{R_1 * R_2}{R_1 + R_2} = \frac{5\Omega * 10\Omega}{(5 + 10)\Omega} = 3.33\Omega$$

$$\tau = R_{eq}C = 3.33\Omega * 0.2F = 0.67s$$

Tips 2:

Remove voltage source to find equivalent resistance, R_{eq} .

SOLUTION 1

Step 3: Find final voltage across capacitor when $t = \infty$.

Below is the circuit when switch is closed for $t > 0.5$ s.

Tips 2:

At dc steady state, capacitor is an open circuit.

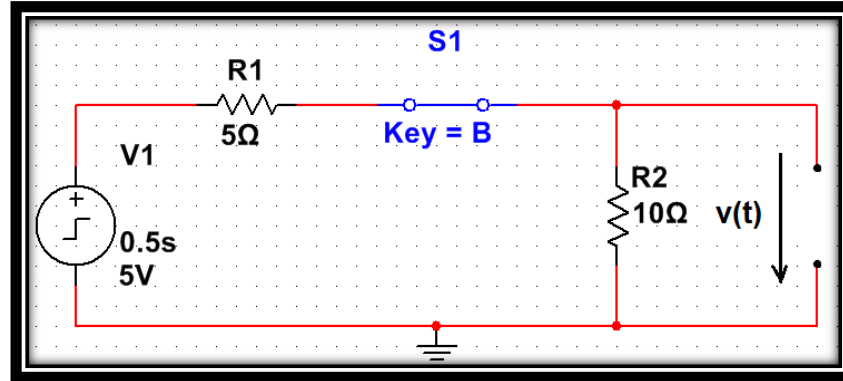


Figure 14

$$v(\infty) = \frac{R_2}{R_2 + R_1} V_1 = \frac{10\Omega}{(10 + 5)\Omega} 5V = 3.33V$$

SOLUTION 1

Step 4: Find voltage across capacitor when
 $t > 0.5$ s.

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(t) = (3.33 - 3.33e^{-1.5t})V$$

OUTPUT RESPONSE 1

Voltage response of an RC circuit in Figure 15:

V(1) : Step function as voltage source

V(5) : Voltage response across capacitor

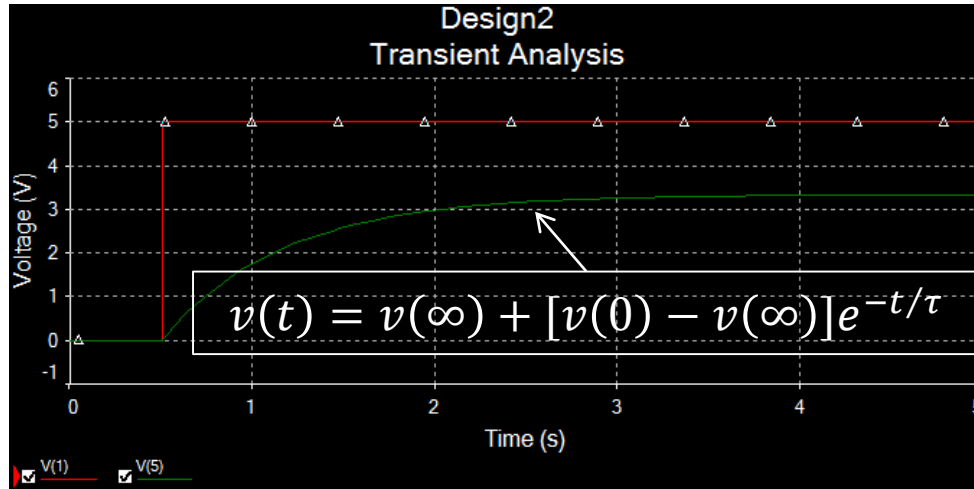


Figure 15

SELF REVIEW QUESTIONS

1. Switch Function is also known as _____
 a) Unit Step Function
 b) Singularity Function
 c) Unit Ramp Function
 d) Unit Impulse Function

2. State the behavior of step response of RC circuit.

Answer: _____

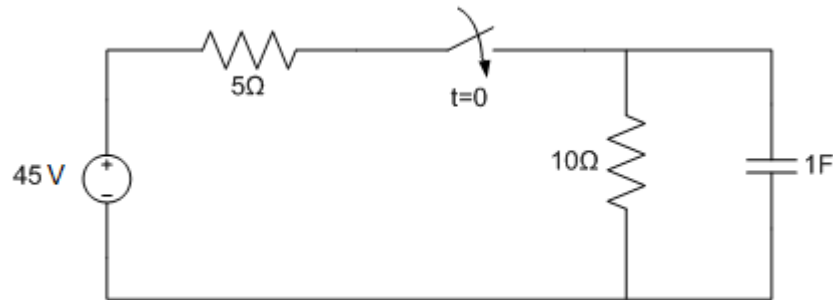


Figure 16

3. Find $v(\infty)$ for circuit in Figure 16.
 a) 30 V b) 35 V
 c) 60 V d) 65 V
4. Find the time constant, τ in Figure 16.
 a) 4.44 s b) 3.33s
 c) 5.55 s d) 2.22 s
5. Based on circuit in Figure 16, calculate the time required to reach half of its steady state value?
 a) 1.23 s b) 2.31 s
 c) 3.12 s d) 1.32 s

ANSWERS

1. b
2. Natural response and steady state response
3. a
4. b
5. b