

ADVANCED ELECTRICAL CIRCUIT

BETI 1333

FIRST ORDER STEP RESPONSE RL CIRCUIT

Suziana binti Ahmad
suziana@utem.edu.my

LESSON OUTCOMES

At the end of this chapter, students are able:



to describe first order step response RL circuit



to illustrate output response of first order step response RL circuit

SUBTOPICS

Step
Response RL
Circuit



Application
of RC and RL
Circuit





INTRODUCTION

What?

1. Source is applied to the circuit


2. Contains several resistors and an inductor

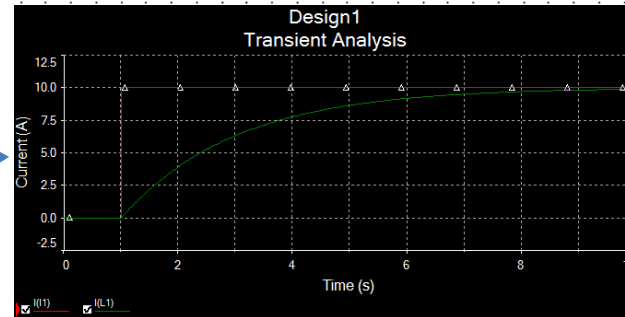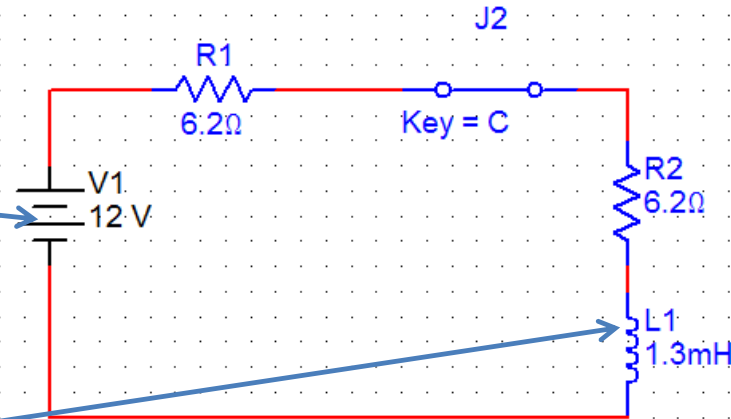3. Output response = Transient and steady-state response



STEP RESPONSE RL CIRCUIT



A switch is closed when $t = 0$

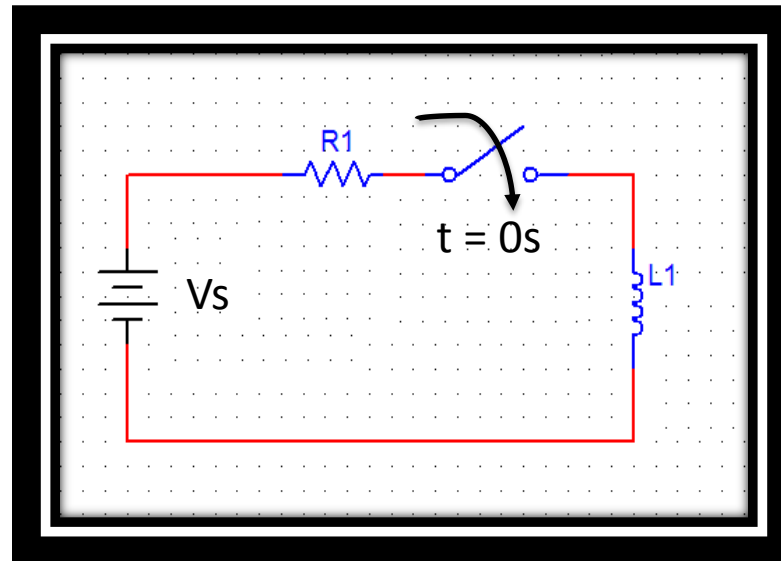

STEP RESPONSE RL CIRCUIT

Step 1: When $t = 0^-$

Step 2: When $t = 0^+$

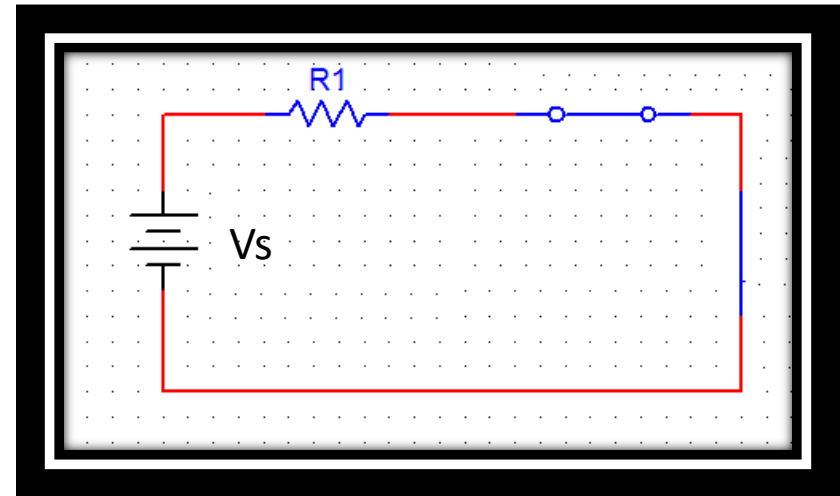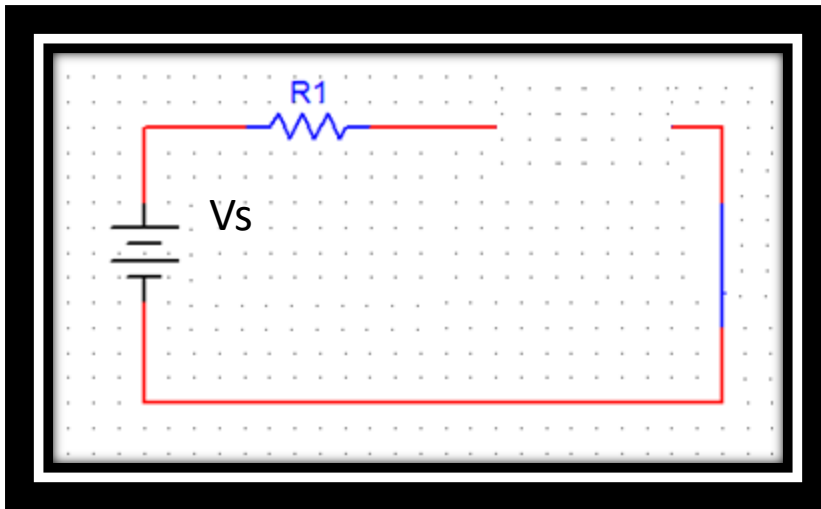

$$i_L = 0 \text{ A}$$


$$i_L = 0 \text{ A}$$

Initial current

Step 3: When $t = \infty$

$$i_L = V_s / R_1$$

Final current

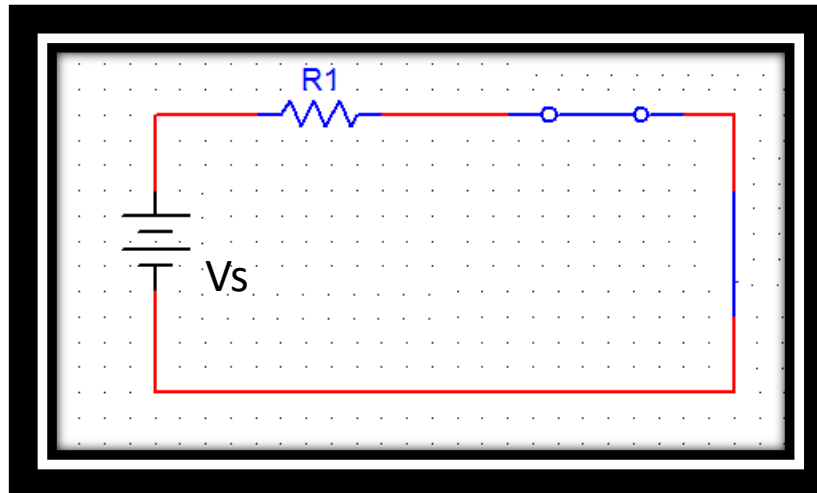

STEP RESPONSE RL CIRCUIT

Current response of an RL circuit:

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$


Final current
through
inductor, when
 $t = \infty$

Initial current
through
inductor, when
 $t = 0$

Time constant
($\tau = \frac{L}{R}$)

EXAMPLE 1

The switch is at position a for a long time before it moves to position b.
Find $i(t)$ for $t > 0$.

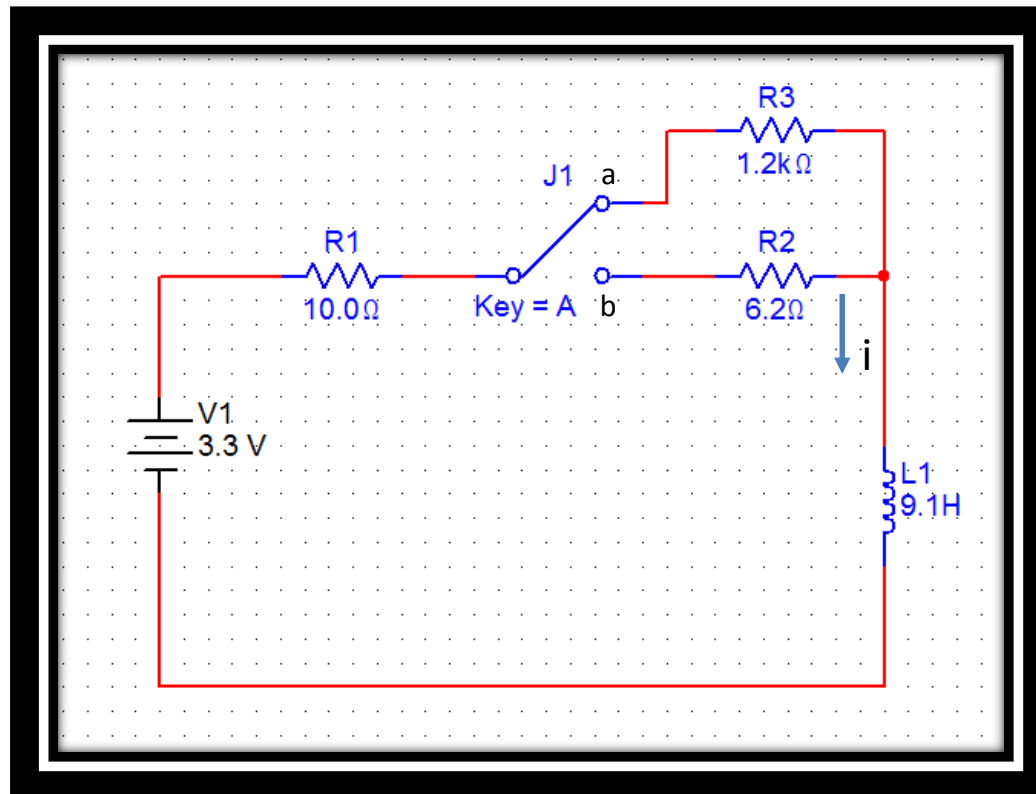


EXAMPLE 1

STEP 1 :

When $t < 0s$:

$$\begin{aligned} i(0) &= V1/R \\ &= 3.3V/1210 \Omega \\ &= 2.73mA \text{ (initial value)} \end{aligned}$$

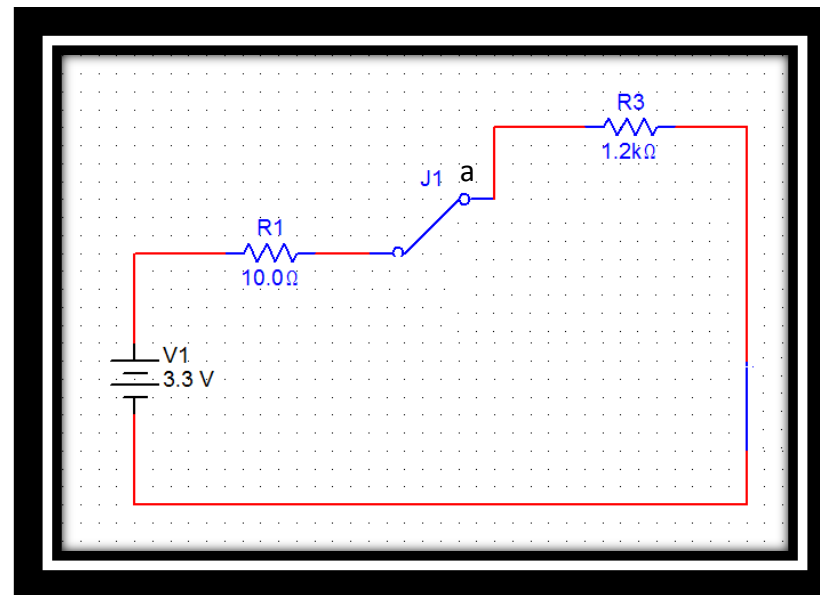


EXAMPLE 1

STEP 2 :

When $t = 0s$: $i(0) = 2.73mA$

When $t > 0s$:

$$\begin{aligned}
 i(\infty) &= V1/R \\
 &= 3.3V/16.2 \Omega \\
 &= 203.7mA
 \end{aligned}$$

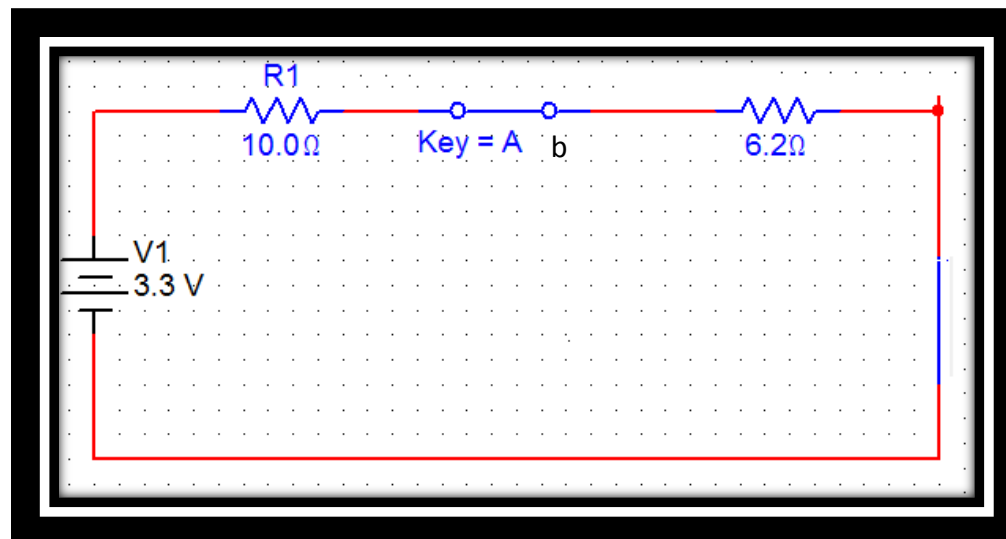

EXAMPLE 1


STEP 3 :

$$\tau = \frac{L}{R}$$

$$= 9.1\text{H} / 16.2\Omega$$

$$= 0.562\text{s}$$

$$R = 10 + 6.2 = 16.2\text{ Ohm}$$

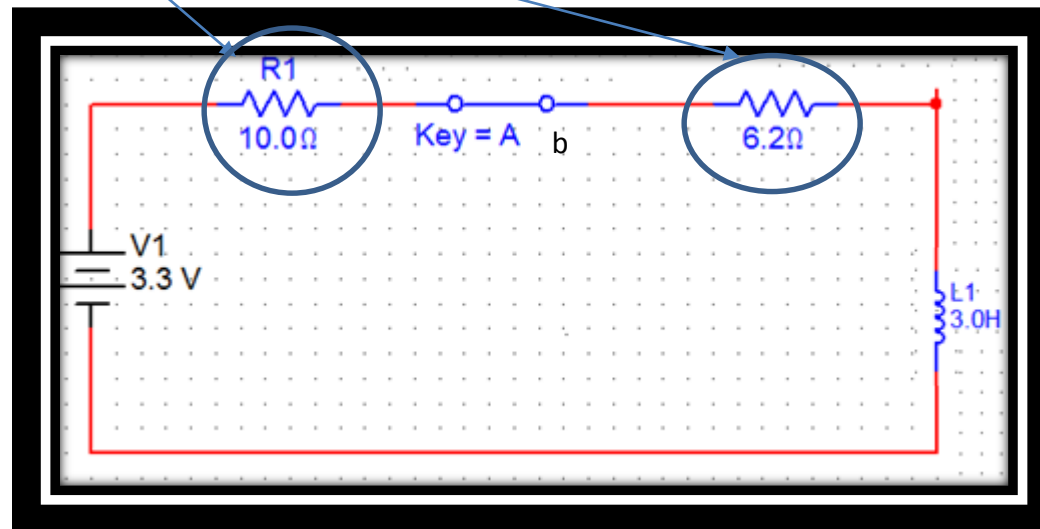


EXAMPLE 1

STEP 4 :

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$


$$i(t) = 203.7m + [2.37m - 203.7m] e^{-1.78t}$$

$$i(t) = 203.7 - 201.3e^{-1.78t} \text{ mA}$$

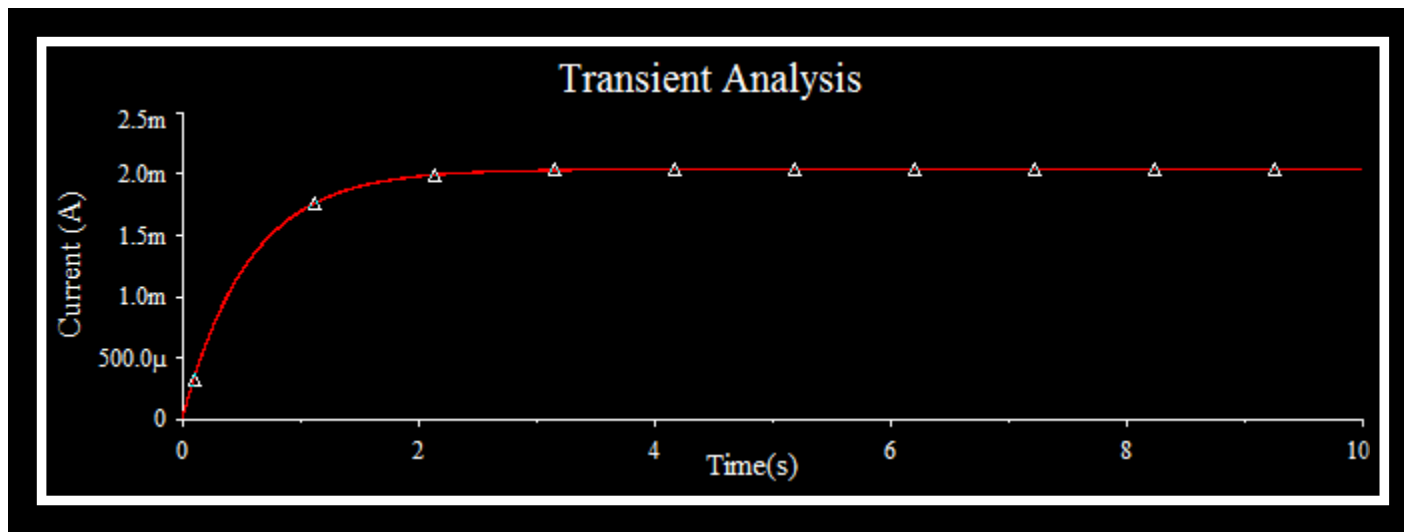

EXAMPLE 2

The switch is closed at $t = 0$ s. Find $i(t)$ for $t > 0$ s.

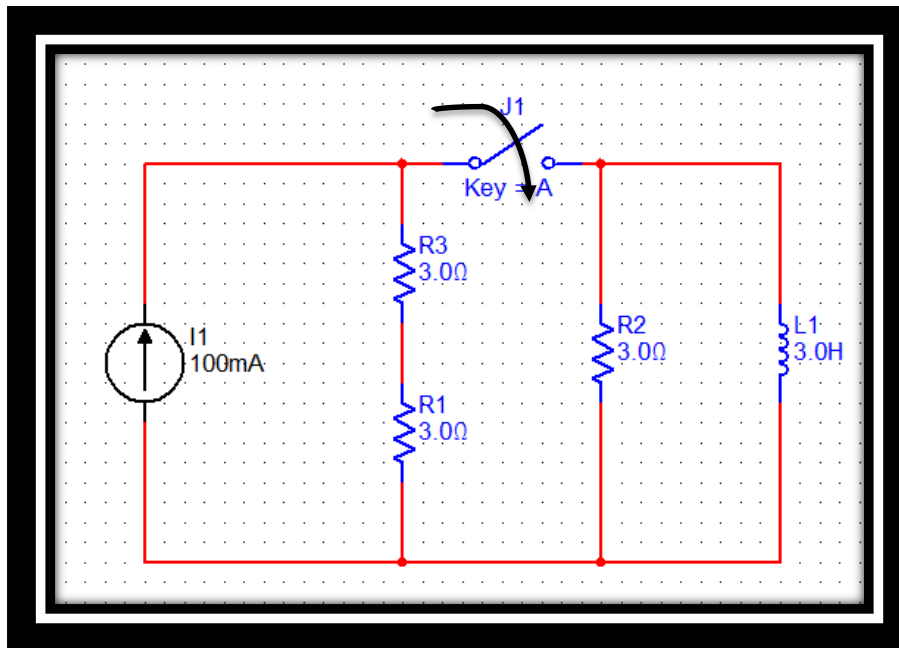


EXAMPLE 2

STEP 1 :

When $t < 0s$:

$i(0) = 0A$ (initial value)

The switch is
opened at $t < 0s$

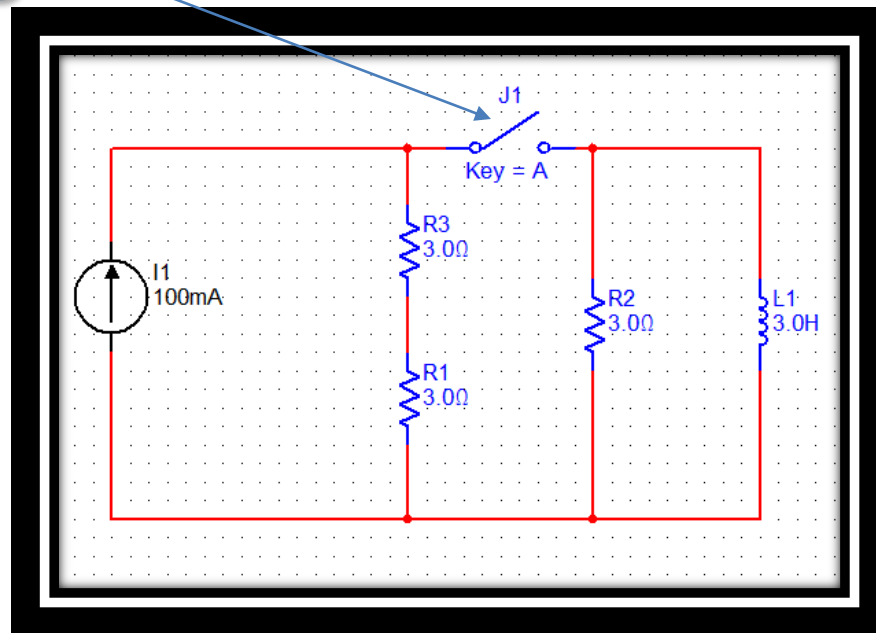

EXAMPLE 2

STEP 2 :

When $t = 0s$: $i(0) = 0A$


When $t > 0s$:

$$R_{eq} = (1/6\Omega + 1/3\Omega)^{-1}$$

$$= 2\Omega$$

$$i(\infty) = 100mA$$

The switch is closed at $t = 0s$

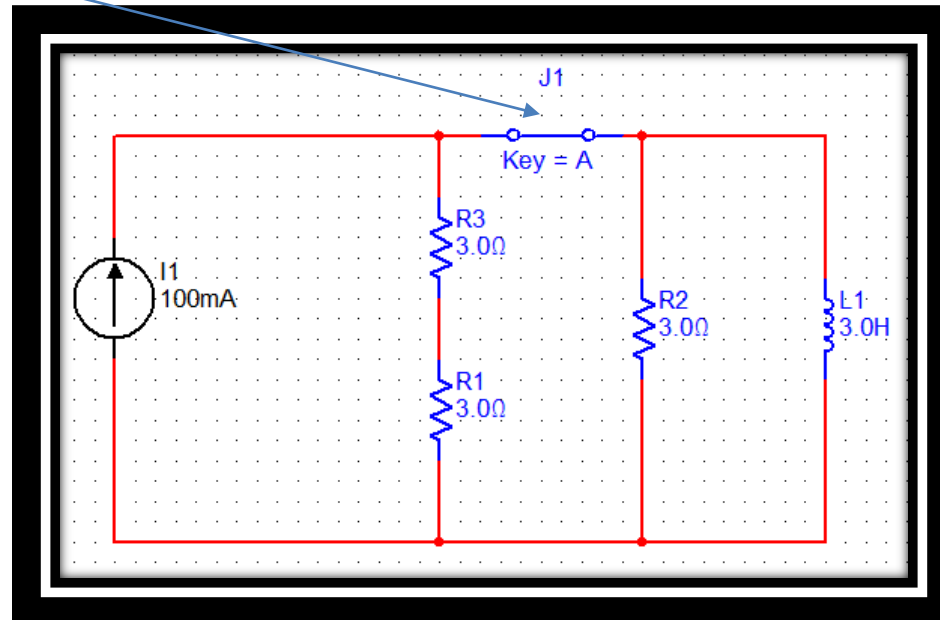


EXAMPLE 2

STEP 3 :

$$\begin{aligned}\tau &= \frac{L}{R_{eq}} \\ &= 3\text{H}/2\Omega \\ &= 1.5\text{s}\end{aligned}$$

$R = (1/6 + 1/3)^{-1} = 2 \text{ Ohm}$

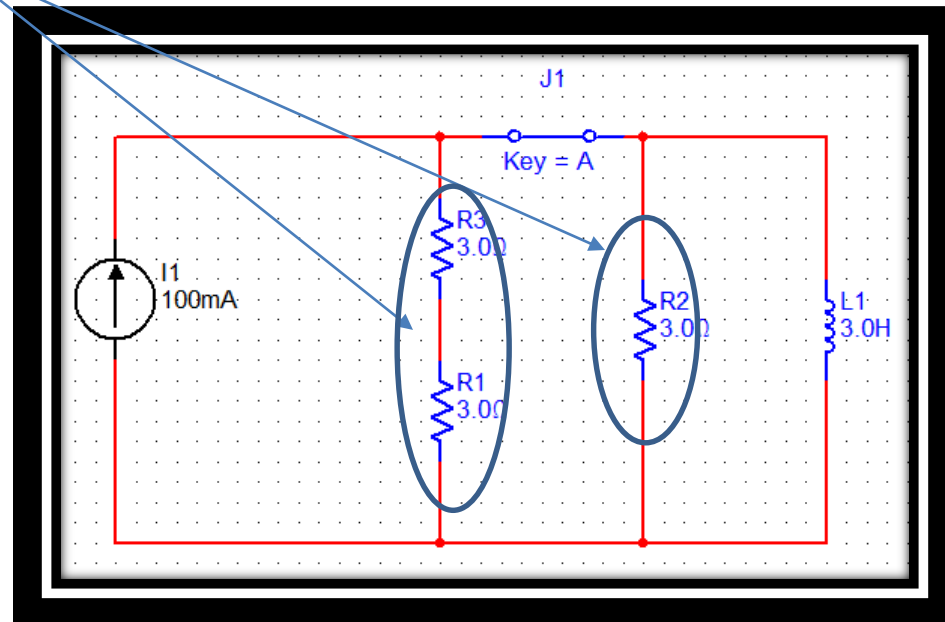

EXAMPLE 2

STEP 4 :

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 100m + [0 - 100] e^{-0.5t}$$


Final current through inductor,
when $t = \infty$

Initial current through inductor,
when $t = 0$


1/ Time constant ($\tau = \frac{L}{R}$)

$$i(t) = 100 - 100 e^{-0.5t} \text{ mA}$$

APPLICATION

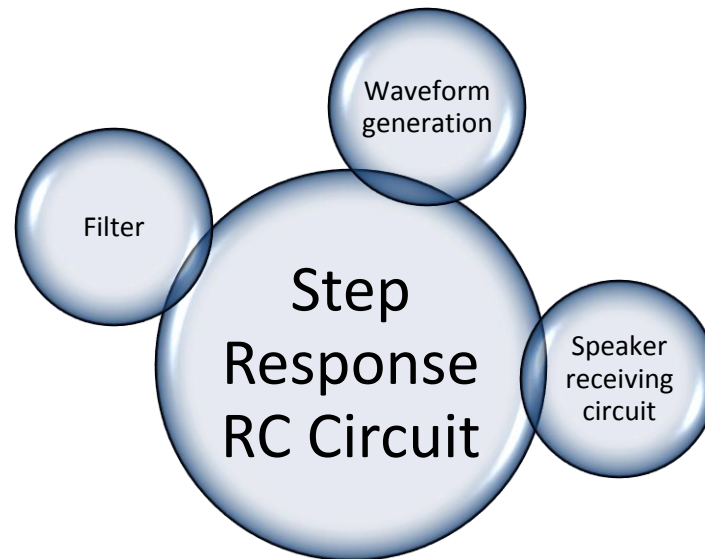

APPLICATION

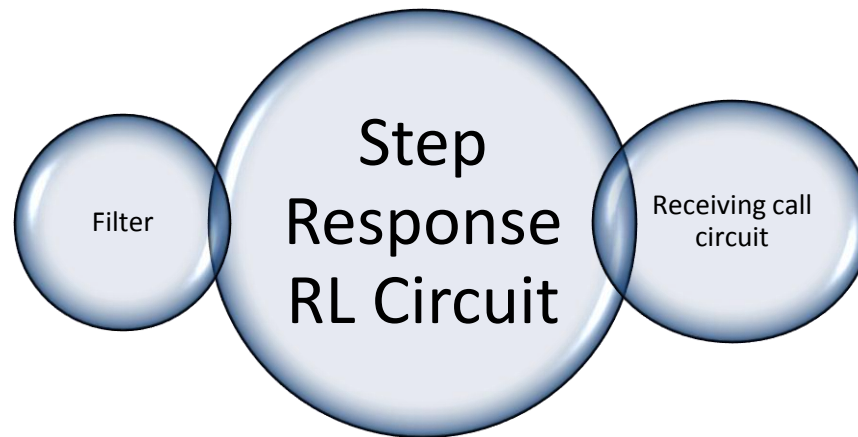

SUMMARY

- Step response circuit requires a source supply.
- RC circuit has better time response during charging and discharging compared to RL circuit.
- Capacitor can handle higher frequency compared to inductor.

SELF REVIEW QUESTIONS

1. A step response circuit has an applied source.

TRUE

☐

FALSE

☐

2. Name a storage element in a first order step response RL circuit.

Answer: _____

3. Given $R = 5\Omega$ and $L = 10H$. What is the time constant for this RL circuit?

a) 0.5s

b) 1s

c) 2s

d) 10s

4. An inductor is connected with 12 Ohm resistor in series. What is the value of inductor that gives the time constant of the circuit is 10ms?

a) 1200mH

b) 0.12H

c) 0.012H

d) 12mH

5. A 5H inductor is connected with 12 Ohm resistor in series in a circuit. The circuit gives time constant of 0.417s. If the time constant need to be increased with the unchanged value of the inductor, the value of the resistor need to be

a) increased

b) unchanged

c) decreased

d) 100 Ohm

ANSWERS

1. TRUE
2. Inductor
3. c
4. b
5. c