

ADVANCED ELECTRICAL CIRCUIT
BETI 1333
STEP RESPONSE PARALLEL RLC CIRCUIT

Halyani binti Mohd Yassim

halyani@utem.edu.my

LESSON OUTCOME

At the end of this chapter, students are able:




to describe second order step response parallel RLC circuit

SUBTOPICS


Step Response
Parallel RLC Circuit



Application of
Second Order
Circuit



STEP RESPONSE PARALLEL RLC CIRCUIT

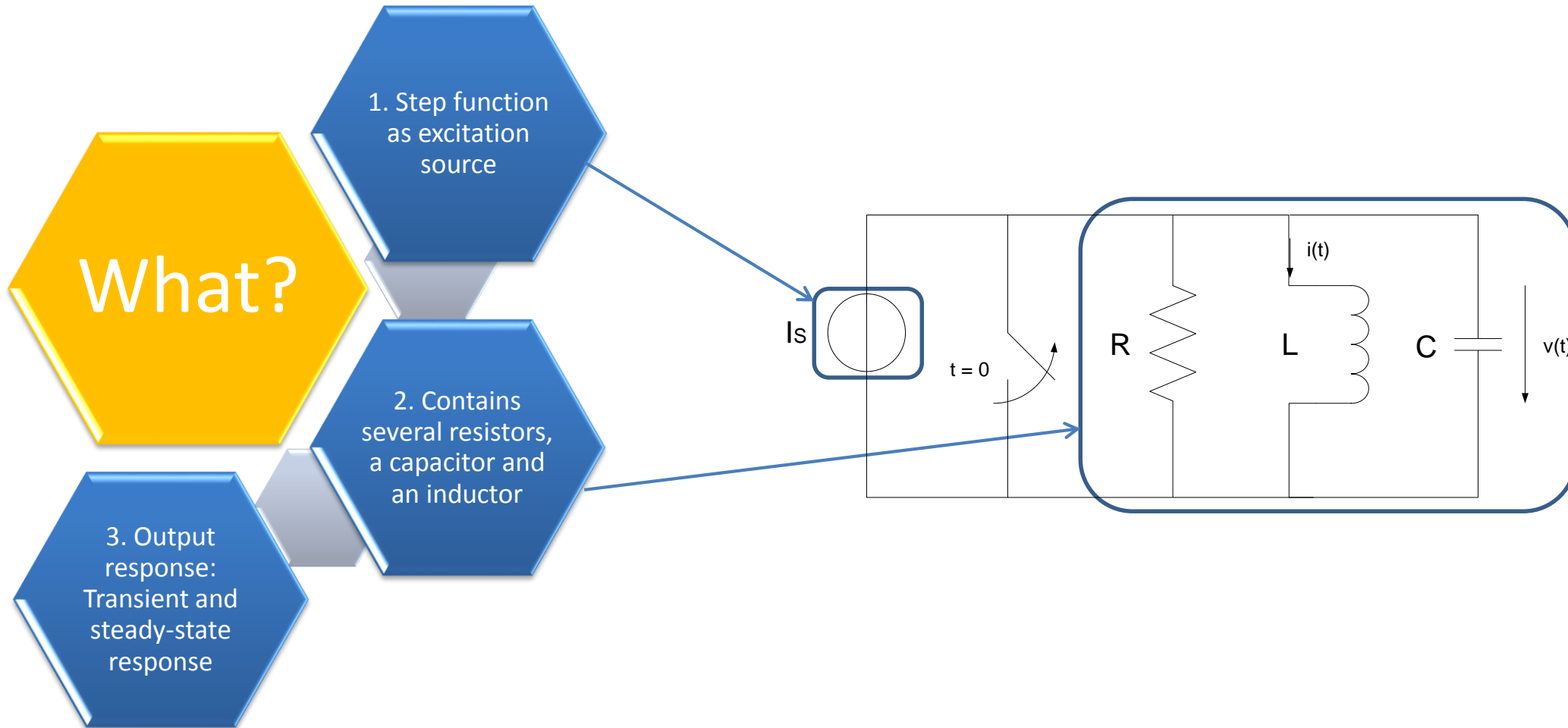

STEP RESPONSE PARALLEL RLC CIRCUIT

Step response parallel RLC Circuit:

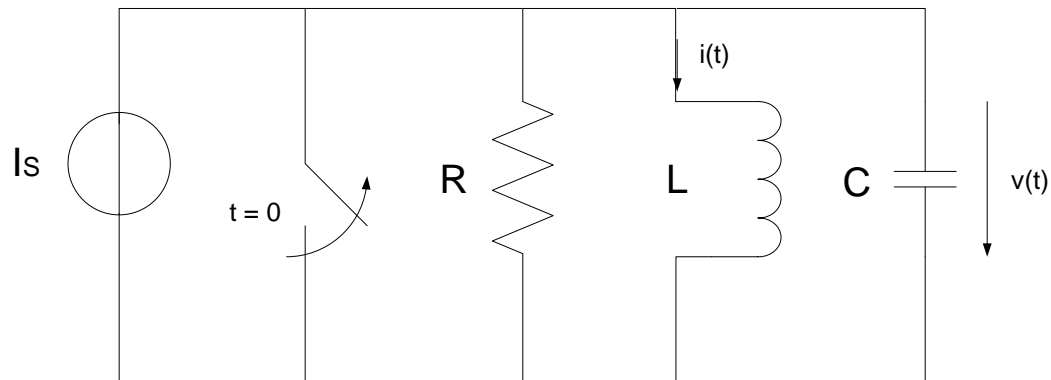


Figure 1

By applying Kirchhoff's Current Law:

$$I_R + I_L + I_C = I_S$$

$$\frac{v}{R} + i + C \frac{dv}{dt} = I_S$$

Second order differential equation:

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{1}{LC} i = \frac{1}{LC} I_S$$

Output response:

$$i(t) = i_T(t) + i_{SS}(t)$$

Transient
response

Steady-state
response
 $i_{SS}(t) = i(\infty)$

STEP RESPONSE PARALLEL RLC CIRCUIT

Types of complete response of step response parallel RLC circuit:

1. Overdamped response ($\alpha > \omega_0$)

$$i(t) = \underbrace{A_1 e^{s_1 t} + A_2 e^{s_2 t}}_{\text{Transient response}} + \underbrace{i(\infty)}_{\text{Steady-state response}}$$

Transient response

Steady-state response

2. Critically damped response ($\alpha = \omega_0$)

$$i(t) = \underbrace{(A_1 + A_2 t) e^{-\alpha t}}_{\text{Transient response}} + \underbrace{i(\infty)}_{\text{Steady-state response}}$$

Transient response

Steady-state response

3. Underdamped response ($\alpha < \omega_0$)

$$i(t) = \underbrace{e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)}_{\text{Transient response}} + \underbrace{i(\infty)}_{\text{Steady-state response}}$$

Transient response

Steady-state response

Note:

1. A_1 and A_2 can be determined from the initial conditions namely $i(0)$ and $\frac{di(0)}{dt}$.

$$\frac{di(0)}{dt} = \frac{v(0)}{L}$$

2. $\alpha = \frac{1}{2RC}$, $\omega_0 = \frac{1}{\sqrt{LC}}$

Damping factor

Undamped natural frequency

3. $s_{1,2} = -\alpha \pm \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha \pm j\omega_d$

Roots of the characteristic equation

EXAMPLE 1

The switch in Figure 2 is closed at $t = 0$. Find $i(t)$ for $t > 0$.

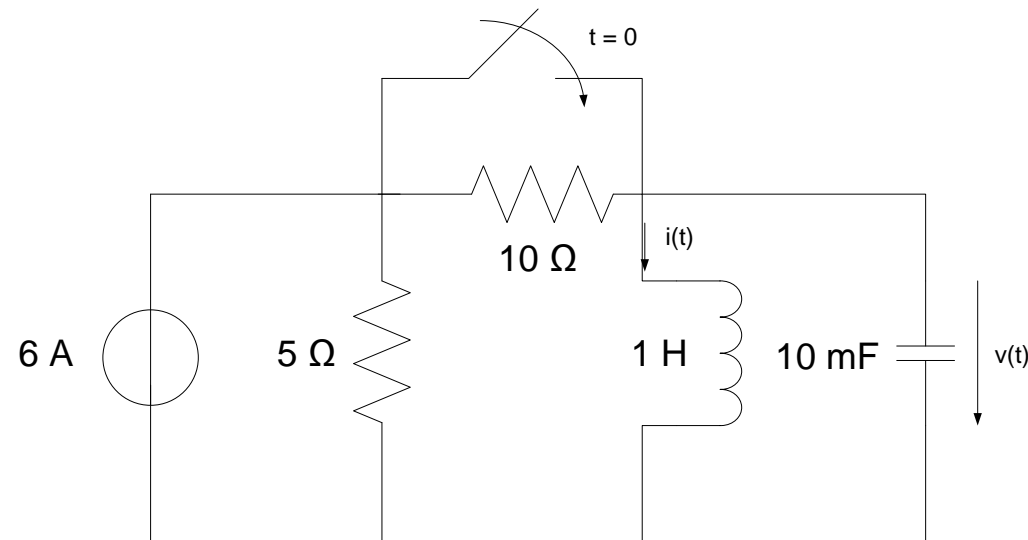


Figure 2

SOLUTION 1

Step 1: Find the initial current across inductor, $i(0)$
 initial voltage across capacitor, $v(0)$ when $t < 0$.

Tips 1:

When $t < 0$, capacitor acts like open circuit and inductor acts like short circuit.

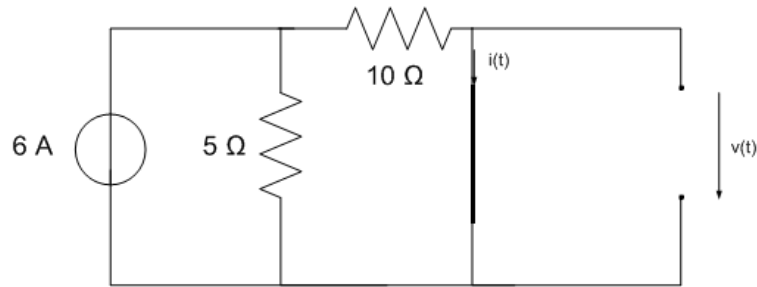


Figure 3

$$i(t) = i(0) = \frac{5 \Omega}{(10 + 5)\Omega} * 6 A = 2 A$$

$$v(t) = v(0) = 0 V$$

SOLUTION 1

Step 2: Determine type of natural response or this circuit, when $t > 0$.

Complete current response for critically damped case:
 $i(t) = (A_1 + A_2 t)e^{-\alpha t} + i(\infty)$

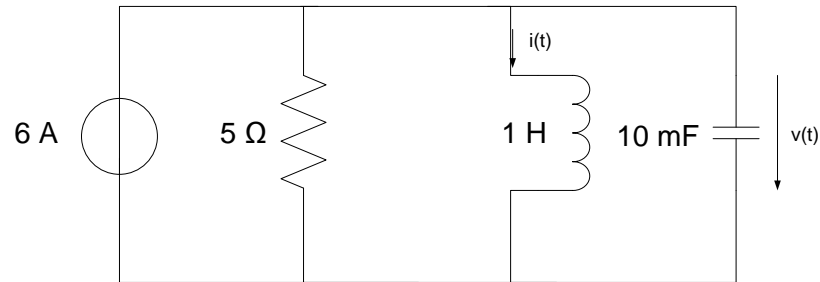


Figure 4

$$\alpha = \frac{1}{2RC} = \frac{1}{2(5)(0.01)} = 10$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1(0.01)}} = 10$$

$\alpha = \omega_0 \rightarrow$ Critically damped response

SOLUTION 1

Step 3: Determine the final value of current through inductor, $i(\infty)$.

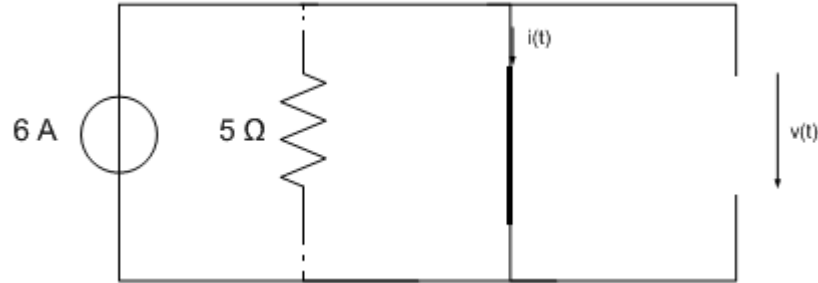


Figure 5

$$i(\infty) = 6 A$$

Tips 2:

At dc steady-state, capacitor acts like open circuit and inductor acts like short circuit.

Tips 3:

Current will flow through less resistance. A 5Ω resistor is short-circuited.

SOLUTION 1

Step 4: Determine A_1 and A_2 from initial conditions

$i(0)$ and $\frac{di(0)}{dt}$, when $t > 0$.

Complete current response:

$$i(t) = 6 + (-4 - 40t)e^{-10t} \text{ A}$$

$$i(0) = (A_1 + A_2(0))e^{-10(0)} + 6 = 2$$

$$A_1 + 6 = 2 \rightarrow A_1 = -4$$

$$\frac{di(0)}{dt} = \frac{v(0)}{L} = 0 \frac{\text{A}}{\text{s}}$$

$$\frac{di}{dt} = A_2 e^{-10t} + (-10)(A_1 + A_2 t)e^{-10t}$$

$$\frac{di(0)}{dt} = A_2 e^{-10(0)} + (-10)(-4 + A_2(0))e^{-10(0)} = 0$$

$$\rightarrow A_2 = -40$$

EXAMPLE 2

The switch in Figure 6 is closed at $t = 0$. Find $i(t)$ for $t > 0$.

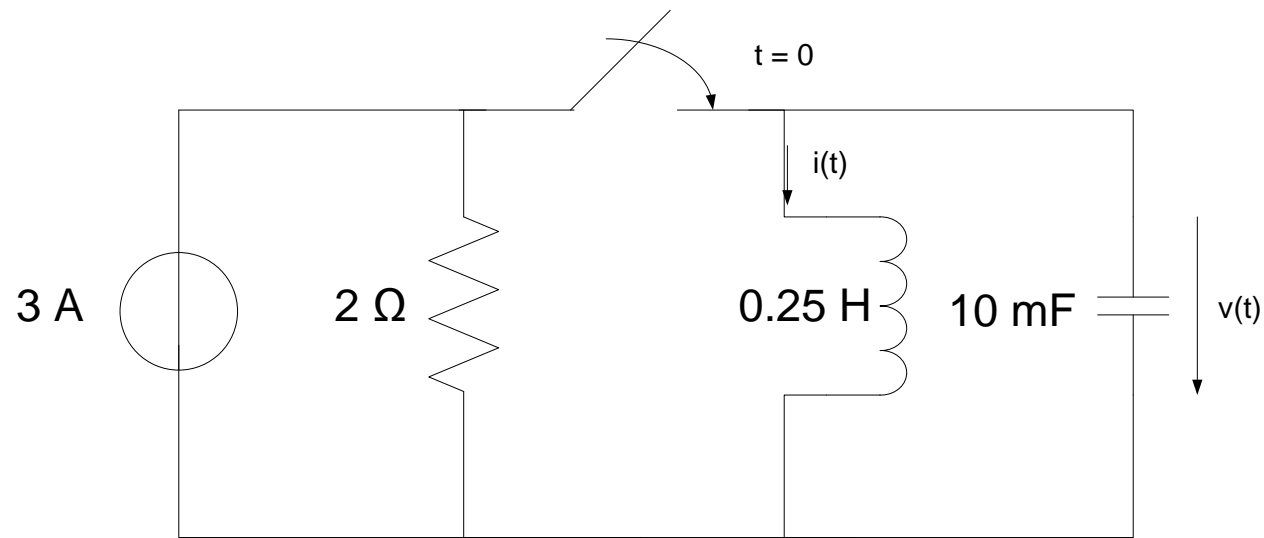


Figure 6

SOLUTION 2

Step 1: Find the initial current across inductor, $i(0)$
 initial voltage across capacitor, $v(0)$ when $t < 0$.

Tips 1:
 When $t < 0$, capacitor acts like open circuit and inductor acts like short circuit.

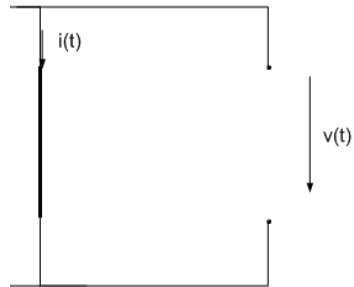


Figure 7

$$i(t) = i(0) = 0 \text{ A}$$

$$v(t) = v(0) = 0 \text{ V}$$

SOLUTION 2

Step 2: Determine type of natural response or this circuit, when $t > 0$.

Complete current response for overdamped case:
 $i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i(\infty)$

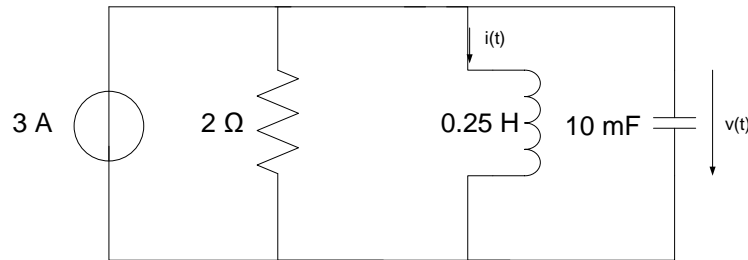


Figure 8

$$\alpha = \frac{1}{2RC} = \frac{1}{2(2)(0.01)} = 25$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.25(0.01)}} = 20$$

$\alpha > \omega_0 \rightarrow$ Overdamped response

SOLUTION 2

Step 3: Determine roots of the characteristic equation, $s_{1,2}$ when $t > 0$.

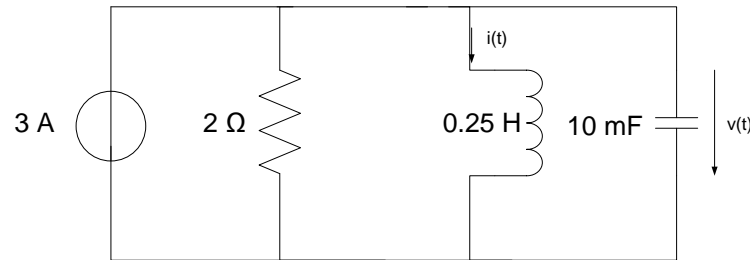


Figure 9

$$s_{1,2} = -\alpha \pm \sqrt{-(\omega_0^2 - \alpha^2)} = -25 \pm \sqrt{-(20^2 - 25^2)}$$

$$s_{1,2} = -10, -40$$

SOLUTION 2

Step 4: Determine the final value of current through inductor, $i(\infty)$.

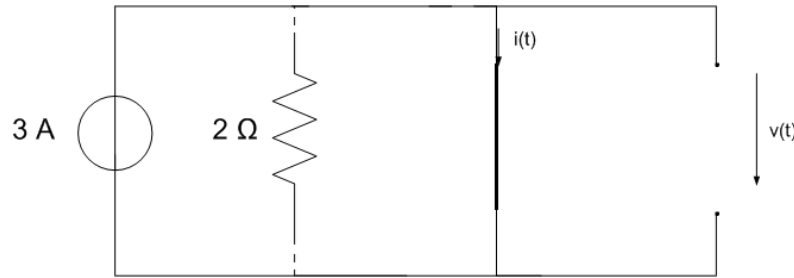


Figure 5

$$i(\infty) = 3 A$$

Tips 2:

At dc steady-state, capacitor acts like open circuit and inductor acts like short circuit.

Tips 3:

Current will flow through less resistance. A 2Ω resistor is short-circuited.

SOLUTION 2

Step 5: Determine A_1 and A_2 from initial conditions

$i(0)$ and $\frac{di(0)}{dt}$, when $t > 0$.

$$-10(-3 - A_2) - 40A_2 = 0 \rightarrow A_2 = 1$$

$$\rightarrow A_1 = -4$$

Complete current response:

$$i(t) = 3 - 4e^{-10t} + e^{-40t} \text{ A}$$

$$i(0) = A_1e^{-10(0)} + A_2e^{-40(0)} + 3 = 0$$

$$A_1 + A_2 + 3 = 0 \rightarrow A_1 = -3 - A_2$$


$$\frac{di(0)}{dt} = \frac{v(0)}{L} = 0 \frac{\text{A}}{\text{s}}$$

$$\frac{di}{dt} = -10A_1e^{-10t} - 40A_2e^{-40t}$$

$$\frac{di(0)}{dt} = -10A_1e^{-10(0)} - 40A_2e^{-40(0)} = 0$$

$$-10A_1 - 40A_2 = 0$$

APPLICATION

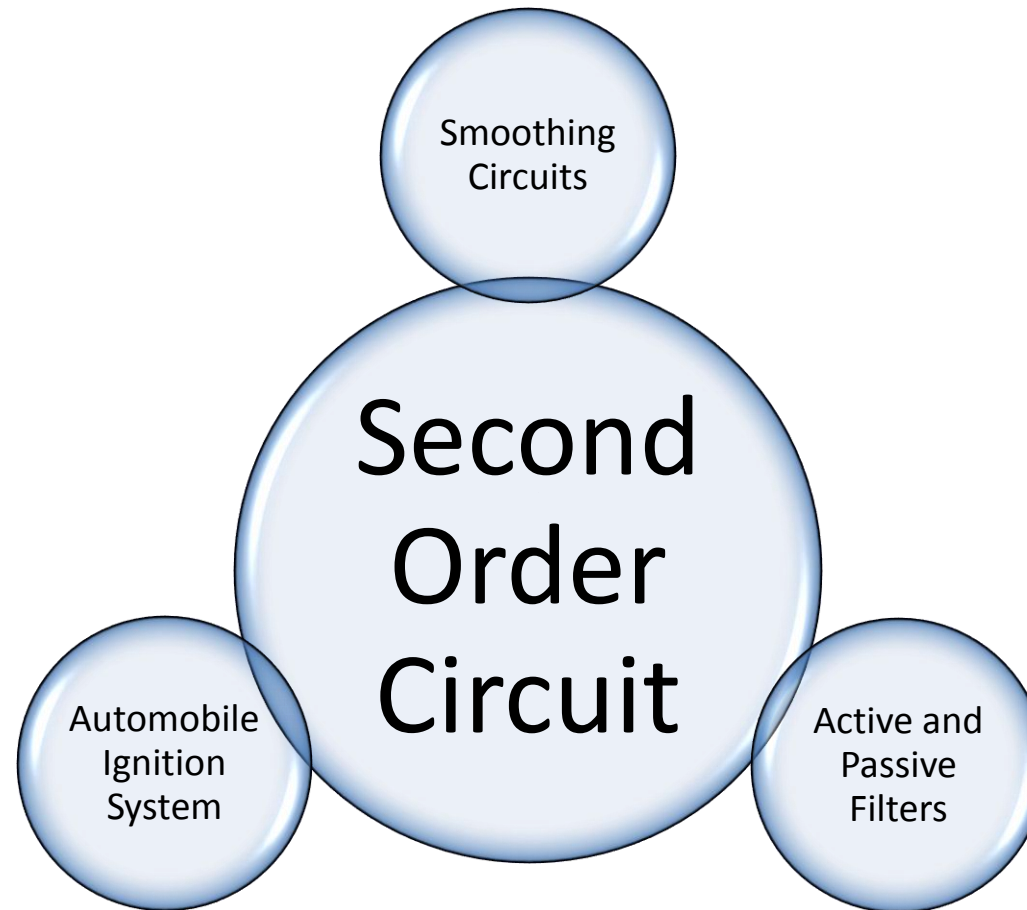

SELF REVIEW QUESTIONS

- The initial voltage in a step response parallel RLC circuit is found by:
 - Replacing capacitor with open circuit
 - Replacing inductor with open circuit
 - Replacing capacitor with short circuit
 - Replacing inductor with short circuit
- The final current in a step response parallel RLC circuit is found by:
 - Replacing capacitor with open circuit
 - Replacing inductor with open circuit
 - Replacing capacitor with short circuit
 - Replacing inductor with short circuit
- Which one is CORRECT about underdamped response:
 - $\alpha < \omega_0$
 - $\alpha > \omega_0$
 - $\alpha = \omega_0$
 - $\alpha = 0$
- The output response of step response RLC circuit is transient and _____ response.
- Given $R = 4 \Omega$ and $C = 1 \text{ F}$. Find the value of L so that a parallel RLC circuit will produce critically damped response.
 - 640 H
 - 6.4 mH
 - 64 H
 - 640 mH

ANSWERS

1. a
2. d
3. a
4. steady-state
5. c